

Name:

Lab section:

Total score for lab: \_\_\_\_ /10

## Lab 3: AC Phasors

### INTRODUCTION:

In this lab, you will apply your knowledge on phasor techniques to analyze some basic circuits comprising resistors and reactive components (i.e. **inductors**). The objective here is to relate a theoretical understanding of impedance and phase to what can be observed using an oscilloscope. In the process, you will learn how to use a signal generator to output a sinusoid signal and an oscilloscope to measure them.

### Learning outcomes

- ❑ Demonstrate use of a signal generator to output AC signals and an oscilloscope to measure them
- ❑ Explain from observation the dependence of impedance on the AC signal frequency
- ❑ Observe the superposition of multiple frequency sources in a basic circuit with reactive components
- ❑ Appreciate that coaxial cables have **inductances** and explain their effects on AC signals

### REQUIRED MATERIALS:

Hardware:

- 1) Digital multimeter (DMM)
- 2) Cathode ray oscilloscope (CRO)
- 3) Signal generator

Components:

- 1) Set of resistors
- 2) Capacitor and inductor
- 3) Breadboard

### Lab Task 1: Applying phasor techniques using single source

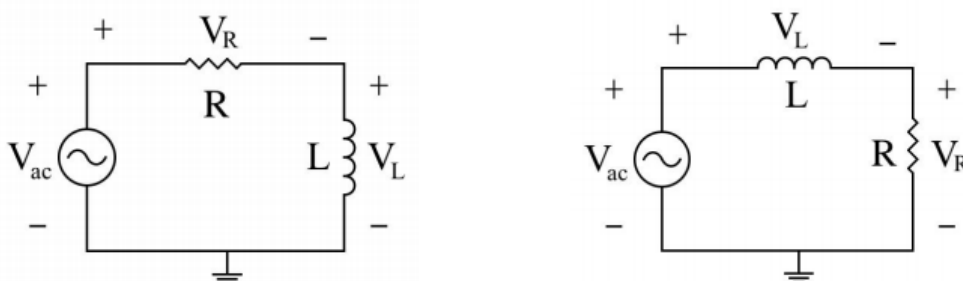


Fig 1a (left) & Fig 1b (right): Schematic of an **RL** circuit

- 1.1 Assemble the circuit of Fig. 1 on a breadboard, given  $V_s = 5 \cos(2\pi f t)$  V,  $R = 1 \text{ k}\Omega$ ,  $L = 10 \text{ mH}$ . Use the signal generator to apply the AC signal ( $V_{ac}$ ), setting the frequency to 2.5kHz. Tune the amplitude of the sine wave until it reaches 5V.
- 1.2 Using the oscilloscope, measure  $V_L$  (using Fig 1a) and  $V_R$  (using Fig 1b) at 10kHz. To measure phase, the wave form of  $V_s$  should also be monitored on the oscilloscope when you measure  $V_L$  and  $V_R$ .
- 1.3 Then set the frequency of the signal generator to 20kHz and measure  $V_L$  and  $V_R$  again.

Table 2: Measured values for Task 1

	Measured $V_L$ (Fig 1a)		Measured $V_R$ (Fig 1b)		I (Calculate using $V_R$ )	
	Amplitude	Phase	Amplitude	Phase	Amplitude	Phase
@ 10kHz						
@ 20kHz						

What is the closest phase of the capacitor voltage relative to the current used in your circuit at 2.5kHz and 5kHz?

For 10 kHz: ☐  $0^\circ$     ☐  $-45^\circ$     ☐  $45^\circ$     ☐  $-90^\circ$     ☐  $90^\circ$

For 20 kHz: ☐  $0^\circ$     ☐  $-45^\circ$     ☐  $45^\circ$     ☐  $-90^\circ$     ☐  $90^\circ$

\_\_\_\_\_ / 4

**Make sure you are graded for Lab Task 1 before moving on to Lab Task 2**

### Lab Task 2: Dual source


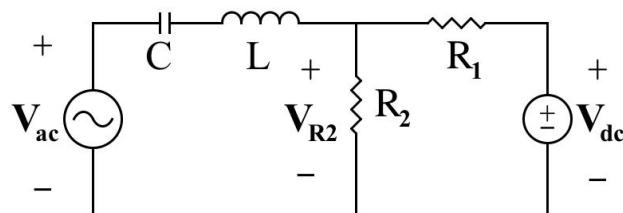


Fig 2: Schematic of circuit with two input sources with different frequencies


- 2.1 Assemble the circuit you have analyzed in Fig. 2 on a breadboard, giving  $R_1 = 1.5 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $L = 10 \text{ mH}$ ,  $C = 68 \text{ nF}$ ,  $V_{ac} = 5 \cos(2\pi ft) \text{ V}$ , and  $V_{dc} = 3 \text{ V}$ . This should only require a small modification of the circuit. Use the power supply to apply a DC voltage of  $V_{dc} = 3 \text{ V}$ .
- 2.2 Keep the amplitude of the AC signal at 5V (same as Lab Task 1) and set the frequency to 10 kHz.
- 2.3 Measure  $V_{R2}$ . Observe the waveform of  $V_{R2}$  in both AC mode and DC mode. You should notice two frequency components on the oscilloscope. The DC component is more distinguishable when you change the oscilloscope setting from AC mode to DC mode. Ask a lab staff to show you how to switch between AC and DC mode on the oscilloscope if you are unsure.
- 2.4 Draw the two waveforms of  $V_{ac}$  and  $V_{R2}$  (in DC mode) in the space provided below. Identify the various frequency components on your graph. Note down the amplitude of the AC wave from  $V_{R2}$  and its phase relative to  $V_{ac}$ .
- 2.5 Then adjust the signal generator frequency to 20 kHz and measure  $V_{R2}$  again.

 **Draw and label  $V_{ac}$  and  $V_{R2}$  at 5 kHz:**



At 5 kHz,  $V_{R2} =$  \_\_\_\_\_ (DC component) + \_\_\_\_\_ (AC component)

 **Draw and label  $V_{ac}$  and  $V_{R2}$  at 20 kHz:**



At 20 kHz,  $V_{R2} =$  \_\_\_\_\_ (DC component) + \_\_\_\_\_ (AC component)

2.6 What is the difference between your results from Lab Task 2 and Lab Task 1?

☐ No difference    ☐ positive DC offset    ☐ negative DC offset    \_\_\_\_\_ / 3

**Make sure you are graded for Lab Task 2 before moving on to the final lab task.**

### Lab Task 3: Co-axial cable capacitance

3.1 Write down the capacitance ( $C_L$ ) and resistance ( $R_L$ ) seen at the input terminals of the CRO. These values can be found around the input socket that connects to the coaxial cable.

$C_L =$  \_\_\_\_\_ pF,  $R_L =$  \_\_\_\_\_ M $\Omega$

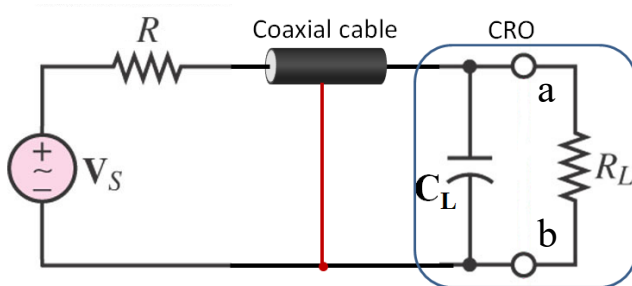


Fig 3a

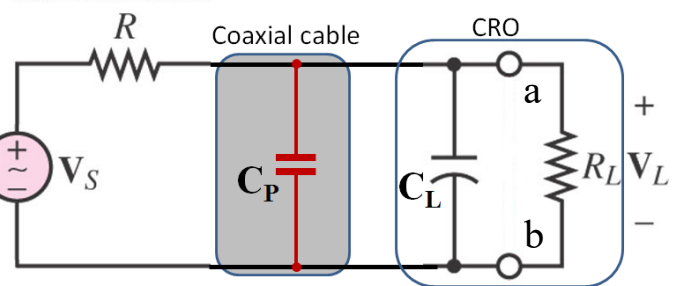


Fig 3b

Assemble a circuit according to Fig 3a where  $R = 1\text{M}\Omega$ . We can represent the coaxial cable by a capacitor  $C_P$  as shown in Fig 3b.  $C_P$  is the total capacitance of the cable, which depends on the length of the cable and its specified capacitance per unit length (pre-lab 3). By estimating the length of the cable, provide an estimate of  $C_P$ .

3.2 **Estimate** the length and thus the total capacitance of your coaxial cable ( $C_P$ ) using the value found in **Pre-lab 3**.

Estimated  $C_P =$  ☐25    ☐50    ☐100    ☐200 pF

Estimated total capacitance across terminals a-b: ☐50    ☐75    ☐125    ☐225 pF

3.3 With  $V_S$  set to 5V peak, answer the following questions.

(a) Measure  $V_L$  when  $V_S$  is set to 100Hz

At 100Hz,  $V_L =$  \_\_\_\_\_ V

(b) Measure  $V_L$  when  $V_S$  is set to 100kHz

At 100kHz,  $V_L =$  \_\_\_\_\_ V

\_\_\_\_\_ / 1

3.4 With  $V_S$  set to 5V peak, answer the following questions.

- (a) At 50 Hz, the impedance across terminals a-b is determined by  $\square R_L \square (C_L + C_P)$  ,  
and a reasonable estimate of this impedance is  
(Hint: Compare the impedances of  $(C_L + C_P)$  and  $R_L$  at 50 Hz. Current prefers a less resistive path.)  
☐  $0\Omega$   
☐  $100k\Omega$   
☐  $1M\Omega$   
☐  $10M\Omega$
- (b) Based on the above estimate of impedance across a-b at 50 Hz, a reasonable estimate of  $V_L$  is  
(Hint: Express  $V_L$  in terms of  $R$ ,  $R_L$ ,  $(C_L + C_P)$  and  $V_S$ . Find  $V_L$  at 50 Hz)  
☐  $0V$   
☐  $0.5V$   
☐  $2.5V$   
☐  $5V$
- (c) At 200 kHz, the impedance across terminals a-b is determined by  $\square R_L \square (C_L + C_P)$  ,  
and a reasonable estimate of this impedance is  
(Hint: Compare the impedances of  $(C_L + C_P)$  and  $R_L$  at 200 kHz. Current prefers a less resistive path.)  
☐  $0\Omega$   
☐  $6k\Omega$   
☐  $60k\Omega$   
☐  $1M\Omega$
- (d) Based on the above estimate of impedance across a-b at 200 kHz, a reasonable estimate of  $V_L$  is  
(Hint: Express  $V_L$  in terms of  $R$ ,  $R_L$ ,  $(C_L + C_P)$  and  $V_S$ . Find  $V_L$  at 200 kHz)  
☐  $0V$   
☐  $0.03V$   
☐  $0.1V$   
☐  $0.5V$

\_\_\_\_\_ / 2