

## Difference Amplifiers

### Q1

For the circuit shown below, assuming the op amp is ideal, and given that  $R_2 = R_4 = 90 \text{ k}\Omega$ ,  $R_1 = R_3 = 10 \text{ k}\Omega$ ,  $v_1 = 1 \text{ V}$  and  $v_2 = 2 \text{ V}$ ,

- Find  $I_1$  and  $I_2$ ;
- Find  $v_a$  and  $v_b$ ;
- Find  $I_3$ ,  $I_F$  and  $v_o$ .

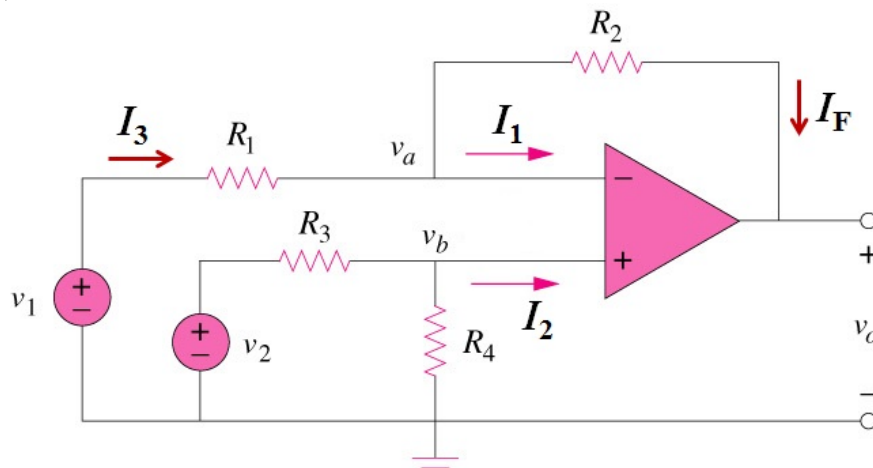


Figure for Q1

### Q2

For the circuit shown below, assuming the op amp is ideal,

- Find the voltage at the input terminals by applying nodal analysis at the non-inverting input terminal,
- Hence find  $v_o$  by applying nodal analysis at the inverting input terminal.

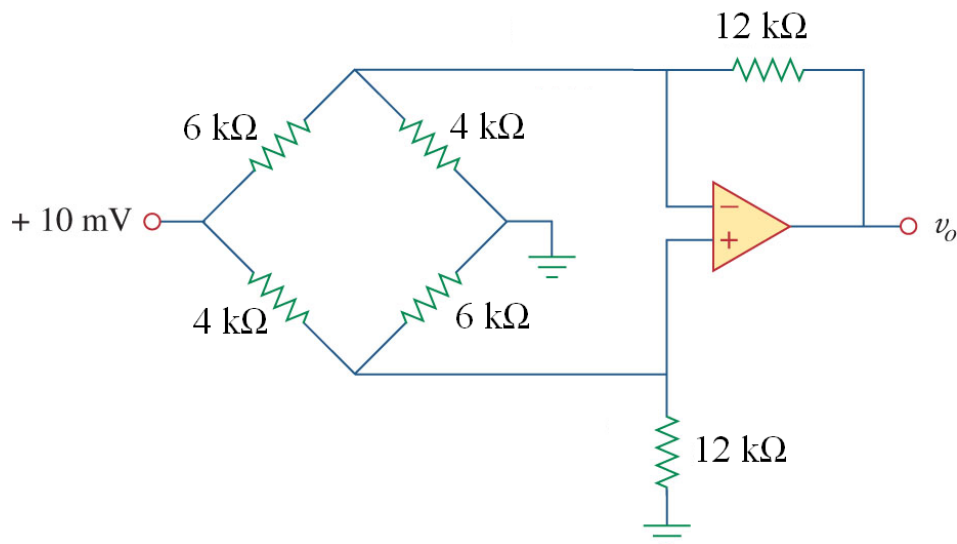


Figure for Q2

## Cascaded Amplifiers

### Q3 [Modified from Alexander Problem 5.57]

For the circuit in Figure 5.84, assuming the op amps are ideal, given  $v_{s1} = 1$  V and  $v_{s2} = 2$  V,

- Find  $i_1$ ,  $i_2$ , and  $v_{o1}$ ;
- Find  $i_3$ ,  $i_4$ , and  $v_{o2}$ ;
- Find  $i_5$ ;
- Hence find  $v_o$ .

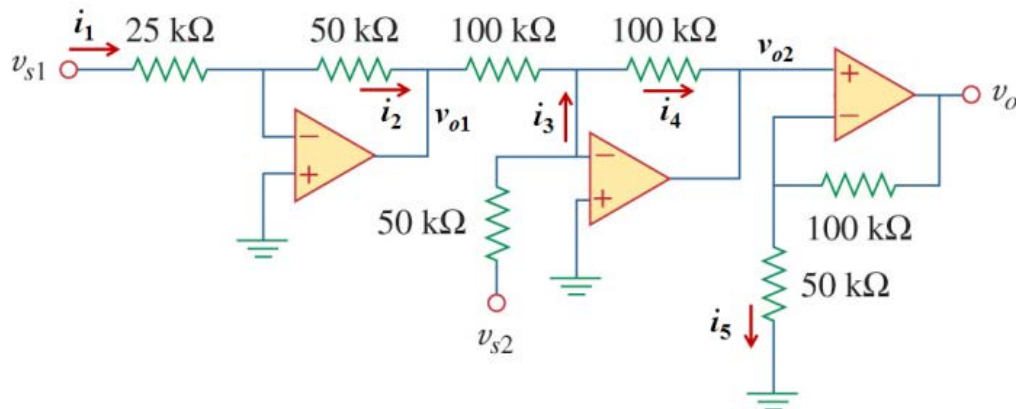


Figure 5.84

### Q4 [Alexander Problem 5.60]

Assuming the op amps are ideal, obtain  $v_o/v_i$  for the circuit in Figure 5.87.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

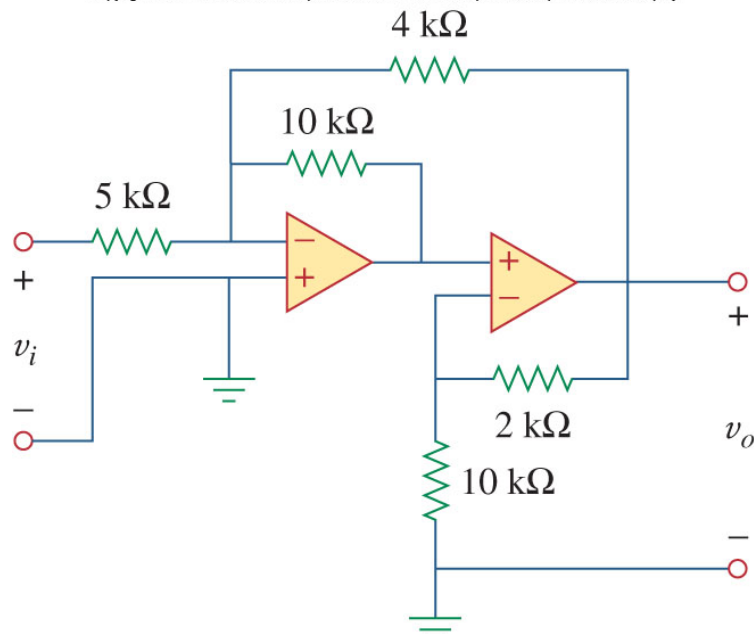


Figure 5.87

## Practical Limits

### Q5

For the circuit below, given  $R_F = 10\text{k}\Omega$ ,  $R_S = 2\text{k}\Omega$ ,  $V_S^+ = 5\text{V}$ , and  $V_S^- = -5\text{V}$ ,

- Find  $V_{\text{out}}$  when  $V_S = 1.2\text{V}$ .
- Sketch the graph of  $V_{\text{out}}$  (y-axis) vs.  $V_S$  (x-axis).

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

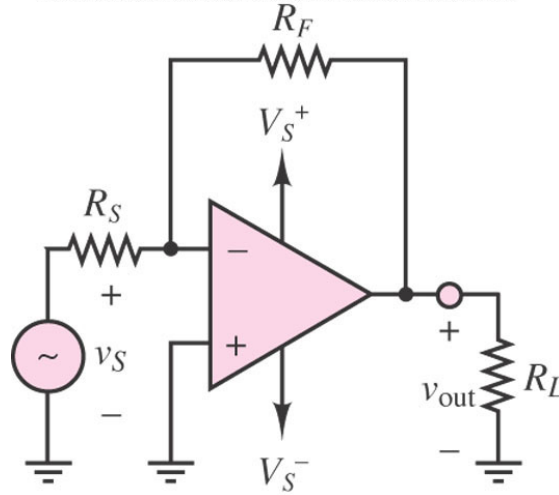


Figure for Q5

**Numerical solutions****Q1**

- a)  $I_1 = 0 \text{ A}$ ,  $I_2 = 0 \text{ A}$
- b)  $v_a = 1.8 \text{ V}$ ,  $v_b = 1.8 \text{ V}$
- c)  $I_3 = -0.08 \text{ mA}$ ,  $I = -0.08 \text{ mA}$ ,  $v_o = 9 \text{ V}$

**Q2**

- a) Input voltages =  $5 \text{ mV}$
- b)  $V_o = 10 \text{ mV}$

**Q3 [Modified from Alexander Problem 5.57]**

- a)  $i_1 = 0.04 \text{ mA}$ ,  $i_2 = 0.04 \text{ mA}$ ,  $v_{o1} = -2 \text{ V}$
- b)  $i_3 = 0.04 \text{ mA}$ ,  $i_4 = 0.02 \text{ mA}$ ,  $v_{o2} = -2 \text{ V}$
- c)  $i_5 = -0.04 \text{ mA}$ ,  $v_o = -6 \text{ V}$

**Q4 [Alexander Problem 5.62]**

Closed loop gain  $v_o/v_i = -0.6 \text{ V}$

**Q5**

- a)  $V_{\text{out}} = -5 \text{ V}$