

Problem Set 7 Hint Sheet**Q1**

Convert source from sinusoid to phasor: $5 \cos(10t + 40^\circ) \rightarrow I_s = 5 \angle 40^\circ \text{ A}$

Note that 3Ω and 0.1F are in series \Rightarrow Impedance $Z = 3 - j3\Omega$

Note that 4Ω , 0.2H and Z are in parallel

We can thus find current through Z using current divider rule:

$$I_o = \frac{1/Z}{(1/Z) + 1/4 + 1/j2} I_s$$

Final step: Convert I_o from phasor into sinusoid


Q2

Convert source from sinusoid to phasor: $20 \sin(100t - 40^\circ) \rightarrow V_s = 20 \angle -130^\circ \text{ V}$

Note that 30Ω and 0.5mF are in series $\Rightarrow Z_x = 30 - j20 \Omega$

Suggested approach to solve: Apply nodal analysis at V_x (see figure below) and then use V_x to find I_x ($I_x = V_x/Z_x$)

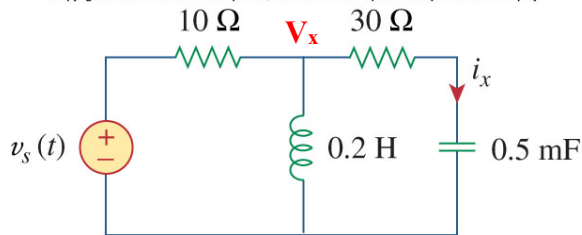Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Nodal equation:

$$\frac{V_x - V_s}{10} + \frac{V_x}{j20} + \frac{V_x}{30 - j20} = 0$$

$$\Rightarrow V_x = 15.643 \angle -114.29^\circ \text{ V}$$

Q3


Apply nodal analysis at node V (i.e. voltage across current source)

$$\frac{V - (120 \angle -15^\circ)}{40 + j20} + \frac{V}{-j30} + \frac{V}{50} + 6 \angle 30^\circ = 0$$

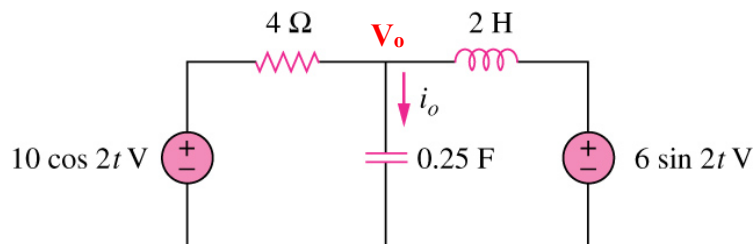Q4

Convert sources from sinusoid to phasor: $10 \cos(2t) \rightarrow 10 \angle 0^\circ$, $6 \sin(2t) \rightarrow 6 \angle -90^\circ$

Work out the impedance values for the inductor and capacitor: $2\text{H} \rightarrow j4$, $0.25\text{F} \rightarrow -j2$



Suggested approach: Apply nodal analysis at V_o (see figure above) and then use V_o to find I_o through the impedance of the 0.25F capacitor.

Nodal equation at node V_o :

$$\frac{V_o - 10\angle 0^\circ}{4} + \frac{V_o}{-j2} + \frac{V_o - 6\angle -90^\circ}{j4} = 0$$


$$\Rightarrow V_o = 2.828\angle -45^\circ$$

Q5

First analyse at DC

Replace 1H inductor with short circuit; Replace AC source with short circuit

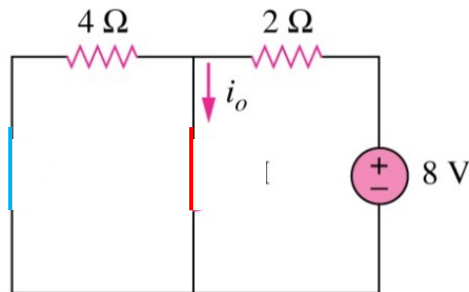Re-draw the circuit, which should look like this:




Observe that in the above circuit, 4Ω is being bypassed and all the current through 2Ω will flow through the inductor path (marked in red).

$$\Rightarrow I_o = 8V/2\Omega$$

Next analyse at AC

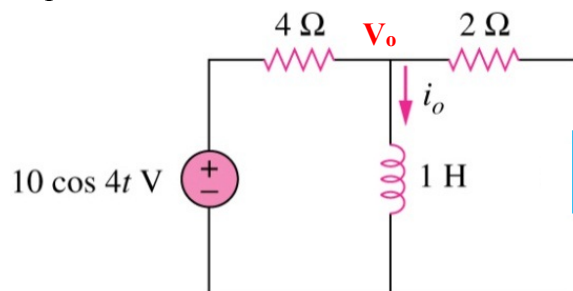Replace DC source with short circuit. Re-draw the circuit, which should look like this:



Convert source from sinusoid to phasor: $10\angle 0^\circ$

Find impedance of 1H inductor: $j4$

Next, solve for I_o . Suggestions to solve for I_o :

Option 1) Find voltage across 1 H by using voltage divider rule noting that 2Ω and 1H are in parallel (impedance: $1.6 + j0.8$), the combination of which is in series with 4Ω :

$$V_o = \left(\frac{1.6 + j0.8}{4 + 1.6 + j0.8} \right) 10$$

Option 2) Find the voltage across 1 H by applying nodal analysis at node V_o :

$$\frac{V_o - 10}{4} + \frac{V_o}{j4} + \frac{V_o}{2} = 0$$

In the above two options, once V_o is known ($3.16\angle 18.44^\circ$ V), I_o can then be derived using the impedance of 1 H ($j4$).

Option 3) Convert the source and $4\ \Omega$ from a Thevenin form to a Norton form (by applying source transformation). This will result in a current source ($2.5\angle 0^\circ\text{ A}$) and all 3 elements in parallel (i.e. $4\ \parallel 2\ \parallel j4$). We can then use current divider rule to find I_o :

Remember to convert your solution from a phasor back into a sinusoid. Then add it to the solution at DC such that final answer as two terms.


Q6

First analyse at DC

Replace inductor with short circuit; Replace capacitor with open circuit

Replace AC current source with open circuit; Replace AC voltage source with short circuit

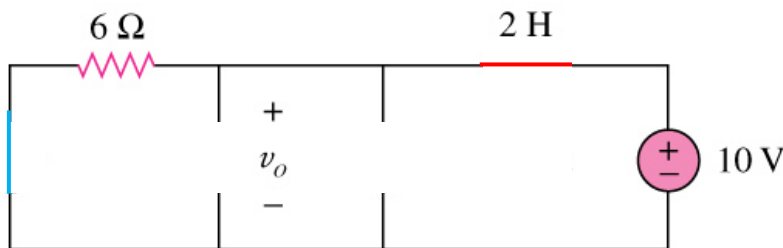Redraw the circuit, which should look like this:




It should be evident that v_o is simply 10 V

Then analyze at 2 rad/s

Replace both the 3 rad/s AC and DC voltage sources with short circuits

Work out the impedance of the capacitor and inductor at 2 rad/s : $2\text{ H} \rightarrow j4\ \Omega$, $1/12\text{ F} \rightarrow -j6\ \Omega$

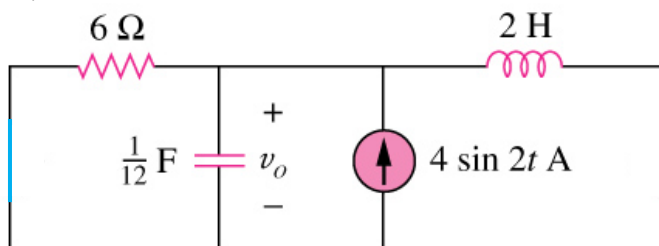Redraw the circuit, which should look like this:



Note that all 3 elements are in parallel with the current source. Hence we can find the total impedance of all 3 elements and use it to find v_o :

$$1/Z = 1/6 + 1/j4 + 1/(-j6) = 1/6 - j/12\text{ S}$$

In this example, there is only one source at 2 rad/s . So we can actually skip converting from sine to cosine as long as we remember that we are using sine as the reference instead of cosine. The final answer for the term at 2 rad/s will then be expressed as a sine.

Using sine as the reference only for 2 rad/s ,

$$V_o = Z \cdot 4\angle 0^\circ = 21.45\angle 26.56^\circ\text{ V}$$


\Rightarrow Convert to sinusoid: $21.45\sin(2t + 26.56^\circ)\text{ V}$

Finally analyze at 3 rad/s

Replace DC voltage source with a short circuit; Replace the 2 rad/s AC current source with an open circuit.

Work out the impedance of the capacitor and inductor at 3 rad/s : $2\text{ H} \rightarrow j6\ \Omega$, $1/12\text{ F} \rightarrow -j4\ \Omega$

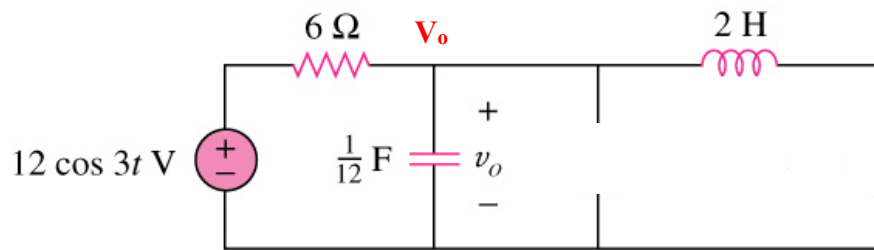Redraw the circuit, which should look like this:



Note that the above circuit is exactly the same as the AC analysis of the previous problem and we so we can use the same three options to find V_o .


Q7

First analyze at DC

Replace 1 rad/s voltage source with short circuit; Replace 3 rad/s current source with open circuit

Replace capacitor with open circuit and inductor with short circuit

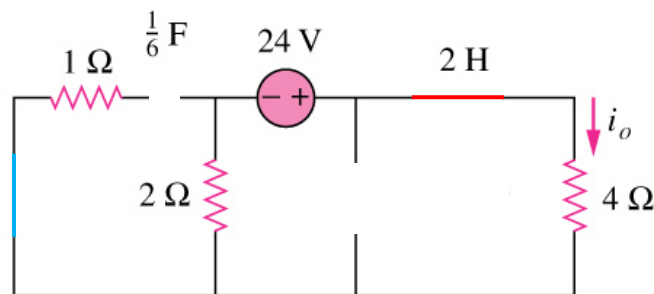Redraw the circuit, which should look like this:




Total loop resistance appearing across 24V DC voltage source = 6Ω

Then analyze at 1 rad/s

Replace 3 rad/s current source with open circuit; Replace DC voltage source with short circuit

Work out impedance of capacitor and inductor at 1 rad/s

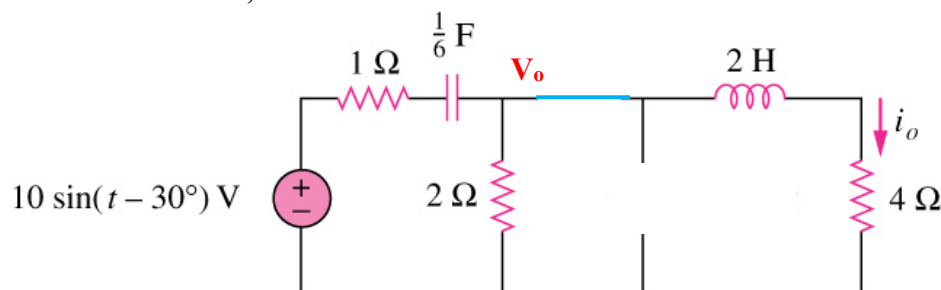Redraw the circuit, which should look like this:



Note that the above circuit is exactly the same as the AC analysis of the Q5 and we so we can use the same three options to find V_o .

Applying nodal analysis at node V_o (using sine as reference),

$$\frac{V_o - 10\angle -30^\circ}{1 - j6} + \frac{V_o}{4 + j2} + \frac{V_o}{2} = 0$$

Solving: $V_o = 2.254 \angle 45.67^\circ \text{ V}$

$I_o = V_o / (4 + j2) = 0.504 \angle 19.1^\circ \text{ A (1 rad/s)}$


Remember to convert your solution from a phasor back into a sinusoid.

Finally analyze at 3 rad/s

Replace 1 rad/s voltage source and DC voltage source with short circuits;

Work out impedance of capacitor and inductor at 3 rad/s: $L \rightarrow j6$, $C \rightarrow -j2$

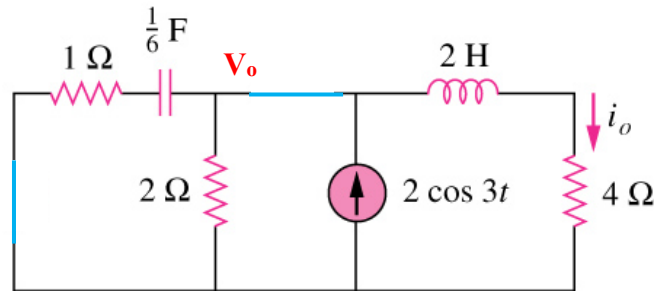Redraw the circuit, which should look like this:



Note that the above circuit is exactly the same as the AC analysis of the Q6 at 2 rad/s and we once again have 3 branches in parallel with the current source. Hence we can find i_o using current divider rule.

Total impedance of 3 branches: $1/Z = 1/2 + 1/(1 - j2) + 1/(4 + j6)$ S

Current divider rule:

$$I_o = \left(\frac{1/(4 + j6)}{1/2 + 1/(1 - j2) + 1/(4 + j6)} \right) 2 \text{ (3 rad/s)}$$

Remember to convert your solution from a phasor back into a sinusoid. Then put together all 3 terms such that final answer has 3 different frequency components.