

Q1

- a) NO current flow in or out of input terminals. $I_1 = I_2 = 0 \text{ A}$
- b) Apply voltage divider rule to find out. $V_b = V_2 \cdot \frac{R_4}{R_3 + R_4} = 2 \cdot \frac{90}{10 + 90} = 1.8 \text{ V};$

The voltage of two input terminals are SAME. $V_a = V_b = 1.8 \text{ V}$

- c) Find I_3 : Apply Mesh Analysis: $I_3 = \frac{(V_1 - V_a)}{R_1} = \frac{1 - 1.8}{10k} = -0.08 \text{ mA}$

Find I_F : $I_F = I_3 = -0.08 \text{ mA}$

Find V_o : Mash Analysis:

$$V_a - V_o = I_F \cdot R_2 \rightarrow V_o = V_a - I_F \cdot R_2 = 1.8 \text{ V} + 0.08 \text{ mA} \cdot 90 \text{ k}\Omega = 9 \text{ V}$$

Q2

- a) As the requirement of the question, using nodal analysis:

$$\frac{V_s - V^+}{4k\Omega} + \frac{0 - V^+}{6k\Omega} + \frac{(0 - V^+)}{12k\Omega} = 0 \rightarrow \frac{V_s}{4k\Omega} = V^+ \left(\frac{1}{4k\Omega} + \frac{1}{6k\Omega} + \frac{1}{12k\Omega} \right) \rightarrow V^+ = \frac{10 \text{ mV}}{\left(1 + \frac{2}{3} + \frac{1}{3}\right)} = 5 \text{ mV}$$

Acturaly, there is a simple method to find out the voltage of input teminals:

$$\text{Apply voltage divider rule: } V^- = V^+ = V_s \cdot \frac{Z_1}{4 + Z_1} = 10 \text{ mV} \cdot \frac{\frac{6 \cdot 12}{6 + 12}}{4 + \frac{6 \cdot 12}{6 + 12}} = 10 \text{ mV} \cdot \frac{1}{2} = 5 \text{ mV}$$

- b) Apply nodel analysis at Node V^- :

$$\frac{(V_o - V^-)}{12k\Omega} + \frac{10 \text{ mV} - V^-}{6k\Omega} + \frac{0 - V^-}{4k\Omega} = 0 \rightarrow V_o = 12k\Omega \cdot \left[V^- \left(\frac{1}{12k\Omega} + \frac{1}{6k\Omega} + \frac{1}{4k\Omega} \right) - \frac{10 \text{ mV}}{6k\Omega} \right]$$

$$V_o = [5 \text{ mV} \cdot (1 + 2 + 3) - 20 \text{ mV}] = 10 \text{ mV}$$

Q3

- a) Find i_1 : Mesh Analysis: $i_1 = \frac{V_{s1} - 0}{25k\Omega} = \frac{1}{25000} = 0.04 \text{ mA}$

Find i_2 : $i_2 = i_1 = 0.04 \text{ mA}$

$$\text{Find } v_{o1}: \text{Mesh Analysis: } \frac{0 - v_{o1}}{50k\Omega} = i_2 \rightarrow v_{o1} = -i_2 \cdot 50k\Omega = -2 \text{ V}$$

- b) Find i_3 : Mesh Analysis: $i_3 = \frac{V_{s2} - 0}{50k\Omega} = \frac{2}{50k\Omega} = 0.04 \text{ mA}$


$$\text{Find } i_4: \text{Node Analysis: } i_4 = \frac{v_{o1} - 0}{100k\Omega} + i_3 = -0.02 \text{ mA} + 0.04 \text{ mA} = 0.02 \text{ mA}$$

$$\text{Find } v_{o2}: \text{Mesh Analysis: } \frac{0 - v_{o2}}{100k\Omega} = i_4 \rightarrow V_{o2} = -i_4 \cdot 100k\Omega = -2 \text{ V}$$

- c) Find i_5 : Mash Analysis: $i_5 = \frac{v_{o2} - 0}{50k\Omega} = -\frac{2}{50k\Omega} = -0.04 \text{ mA}$

- d) Find v_o : Mesh Analysis: $\frac{v_o - 0}{100k\Omega + 50k\Omega} = i_5 \rightarrow v_o = -0.04 \text{ mA} \cdot 150k\Omega = -6 \text{ V}$

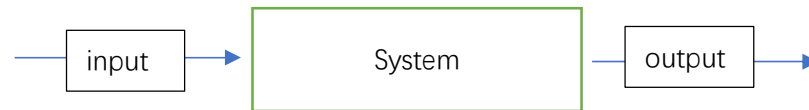Q4 Asking to find out the voltage gain of this circuit.



Point is that building the equation has both v_i and v_o

Assuming the Right Amp is P2, the input terminals are V_2^+ and V_2^- . Also assuming the Left Amp is P1, the input terminals are V_1^+ and V_1^- . From the circuit, we get:

$$V_1^- = V_1^+ = 0 \text{ V.}$$

$$V_2^+ = V_2^- = v_o \cdot \frac{10k\Omega}{10k\Omega + 2k\Omega} = \frac{5}{6} v_o$$

Then apply Node Analysis (KCL) on Node V_1^- :

$$\frac{v_i - 0}{5k\Omega} + \frac{v_o - 0}{4k\Omega} + \frac{V_2^+ - 0}{10k\Omega} = 0$$

$$4v_i + 5v_o + \frac{5}{3}v_o = 0$$

$$\frac{20}{3}v_o = -4v_i$$

$$\frac{v_o}{v_i} = -4 \times \frac{3}{20} = -\frac{6}{10} = -0.6$$

Q5

$$a) \frac{v_s}{R_S} + \frac{v_{out}}{R_F} = 0 \rightarrow v_{out} = -v_s \cdot \frac{R_S}{R_F} = -1.2 \times 5 = -6 \text{ V}$$

However, as this is an active Amp, there is limitation of v_{out} due to the power supply.

$$V_s^+ < v_{out} < V_s^- \rightarrow v_{out} = -5 \text{ V}$$

$$H(j\omega) = -\frac{R_S}{R_F} = -5$$

