

1) For circuit in Fig 1,

3 marks

- Obtain the Norton equivalent to the left of terminals a-b;
- Hence use the result to find current i .

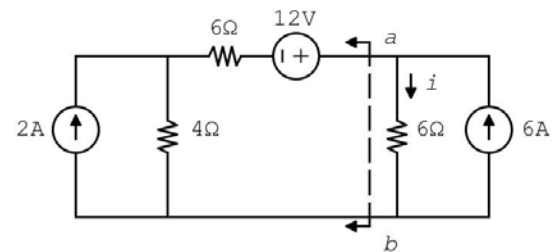


Fig 1

2) By obtaining the Thevenin equivalent of the circuit in Fig 2 seen across R ,

3 marks

- Determine the value of R for maximum power to be delivered to R
- Maximum power delivered

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

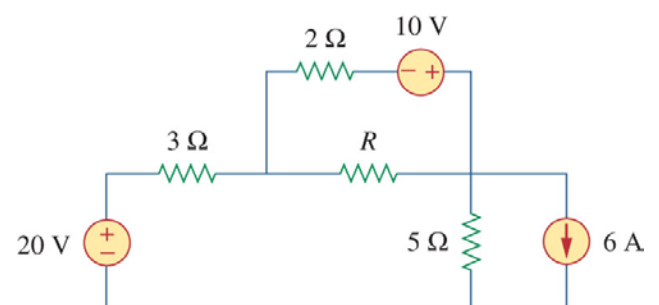


Fig 2

3) For the circuit in Fig 3, find v_1 and v_2 .

4 marks

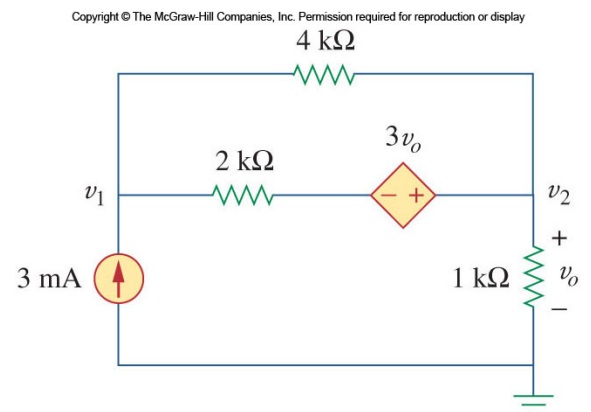


Fig 3

4) Express the following in their polar and Euler forms

3 marks

i) $2\sqrt{3} + 2j = 4\angle 30^\circ = 4e^{(\pi/6)i}$

ii) $-6 - 6j = (6\sqrt{2})\angle -135^\circ = (6\sqrt{2})e^{(-3\pi/4)i}$

iii) $5 - 5\sqrt{3}j = 10\angle -60^\circ = 10e^{(-1\pi/3)i}$

5) Calculating following complex number

3 marks

i) $(8 - 3j) \times (4 + 6j) = 50 + 36j$

ii) $(3 + 5j)/(8 - 2j) = 7/34 + (23/34)j$

iii) $1/(2 - 3\sqrt{3}j) = 2/31 + (3\sqrt{3}/31)j$