

Class Assessment (Week 7)

Started: Oct 13 at 11:11am

Quiz Instructions


Question 1

1 pts

With reference to Fig 1, the circuit's frequency response can be expressed in the form:

$$\frac{V_o}{V_i} = \frac{A}{1 + \frac{j\omega}{\omega_c}}$$

Determine the value of A.

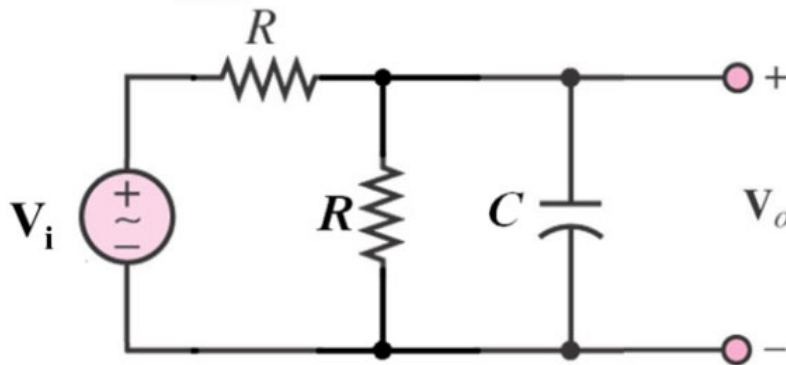

Question 2

1 pts

Choose the correct expression for the cut off radian frequency.

☐ $2/(RC)$

☐ $1/(RC)$

☐ $1/(2RC)$

☐ RC

Question 3**1 pts**

Determine $|V_o/V_i|$ at 0 rad/s.

Question 4**1 pts**

Determine $|V_o/V_i|$ at the cut off radian frequency.

Question 5**1 pts**

Determine $|V_o/V_i|$ in the limit where the frequency is infinitely high.

Question 6**1 pts**

Determine $\angle \left(\frac{V_o}{V_i} \right)$ at 0 rad/s in degrees.

Question 7**1 pts**

Determine $\angle \left(\frac{V_o}{V_i} \right)$ at the cut off radian frequency (in degrees).

Question 8**1 pts**

Determine $\angle \left(\frac{V_o}{V_i} \right)$ in the limit where the frequency is infinitely high (in degrees).

Quiz saved at 6:09pm

[Submit Quiz](#)