

Class Assignment 2 - Solution

1)

a) When $t < 0$, $i(t) = 0$ A.

b) When $t < 0$, $v(t) = 20$ V.

c)

When $t > 0$, the voltage source can be considered as replaced by “short circuit” as $20u(-t) = 0$.

The Norton resistance at the capacitor terminal is

$$R_N = 5 \parallel 10 = \frac{5(10)}{5 + 10} = \frac{10}{3} \Omega$$

and the time constant is

$$\tau = R_N C = \frac{2}{3} s$$

When $t \rightarrow \infty$, the capacitor is fully charged by the current source

$$v(\infty) = 3 \left(\frac{10}{3} \right) = 10V$$

After the switch is closed, $v(t)$ decreases from 20V to 10V → Case B for v_c where $\Delta v = 10V$

$$v(t) = v(\infty) + \Delta v e^{-\frac{t-t_0}{\tau}} = 10 + 10 e^{-\frac{t-0}{2/3}} = 10(1 + e^{-1.5t}) V$$

For $t > 0$, the voltage across the 5Ω resistor is the same as that of capacitor in parallel. The current along the resistor is

$$i(t) = -\frac{v(t)}{5} = -2(1 + e^{-1.5t}) A$$

NOTE

After solving voltage across capacitor by Case A or Case B, current along the capacitor could be evaluated from v . For $t > 0$, to find current along the capacitor:

$$i_c(t) = C \frac{dv}{dt} = C(-15e^{-1.5t}) = -3e^{-1.5t} A$$

OR by KCL :

$$i_c(t) = 3 - \frac{v(t)}{5} - \frac{v(t)}{10} = 3 - 2(1 + e^{-1.5t}) - (1 + e^{-1.5t}) = -3e^{-1.5t} A$$

Class Assignment 2 - Solution

2.

When $t < 0$, $i(t) = 0$ A when both S1 and S2 are open.

For $0 < t < 2$, we evaluate current i_1 along the inductor for S1 is closed and S2 is open.

The Norton resistance at the inductor terminal is

$$R_1 = 15 + 10 + 20 = 45\Omega$$

Time constant is

$$\tau_1 = \frac{L}{R_1} = \frac{5}{45} = \frac{1}{9}s$$

To find the current along the inductor, we assume that S2 remains open

$$i_1(\infty) = 6 \times \frac{15}{15 + 10 + 20} = 2A$$

The current along the inductor can be described with Case A as the current increases for $0 < t < 2$:

$$i_1(t) = i_1(t_0) + \Delta i_1 \left(1 - e^{-\frac{t-t_0}{\tau_1}} \right) = 2(1 - e^{-9t}) A$$

For $t > 2$, S2 is closed and we evaluate current i_2 along the inductor.

The Norton resistance at the inductor terminal is

$$R_2 = 15 + 10 = 25\Omega$$

Time constant is

$$\tau_2 = \frac{L}{R_2} = \frac{5}{25} = 0.2s$$

At $t \rightarrow \infty$, current along the inductor converges to

$$i_2(\infty) = 6 \times \frac{15}{15 + 10} = 3.6A$$

Therefore, for $t > 2$, i_2 increases and Case A applies

Class Assignment 2 - Solution

$$\begin{aligned} i_2(t) &= i_2(t_0) + \Delta i_2 \left(1 - e^{-\frac{(t-t_0)}{\tau}} \right) = i_1(2) + (i_2(\infty) - i_1(2)) (1 - e^{-(t-2)/0.2}) \\ &= (3.6 - 1.6e^{-5(t-2)}) A \end{aligned}$$

Therefore,

$$i(t) = \begin{cases} 0 \text{ A} & , t < 0 \\ 2(1 - e^{-9t}) \text{ A} & , 0 < t < 2 \\ (3.6 - 1.6e^{-5(t-2)}) \text{ A} & , t > 2 \end{cases}$$

$$i(1) = 1.9998 \text{ A}$$

$$i(3) = 3.5892 \text{ A}$$