

Review Questions

Q1. [Rizzoni Problem 2.13]

Use KCL to determine the unknown currents in the following circuit given that $I_0 = -2\text{A}$, $I_1 = -4\text{A}$, $I_S = 8\text{A}$ and $V_S = 12\text{V}$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

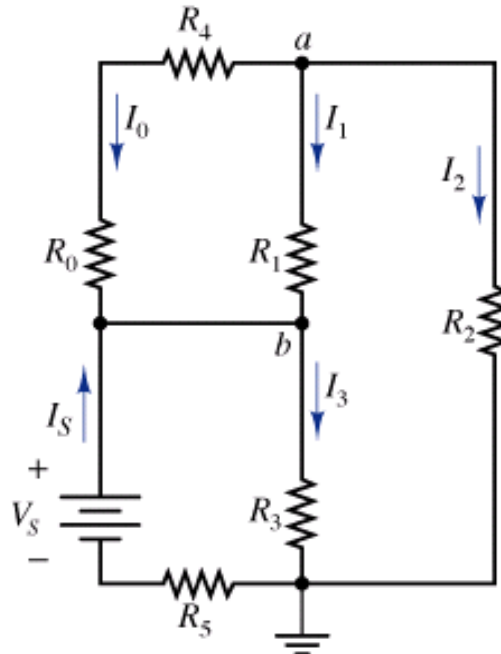


Figure P2.13

Q2. [Rizzoni Problem 2.24]

Apply KVL to Figure P2.24 to find the power dissipated or supplied for each element. Hence determine the amount of power dissipated and supplied overall.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

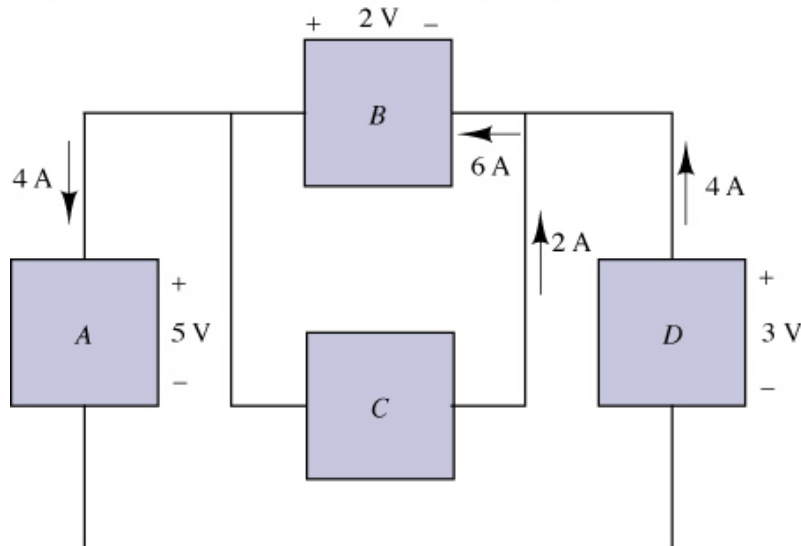


Figure P2.24

Q3. [Alexander Problem 2.12]

With reference to the circuit in Fig 2.76, find v_1 , v_2 , and v_3 by applying KVL.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

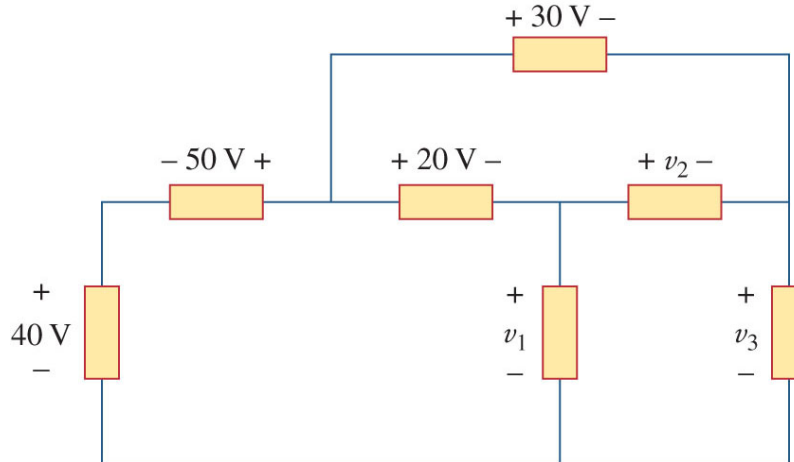


Figure 2.76

Q4. [Rizzoni Problem 2.21]

In the circuit of Figure P2.21, determine the power absorbed by the resistor R and the power delivered by the current source.

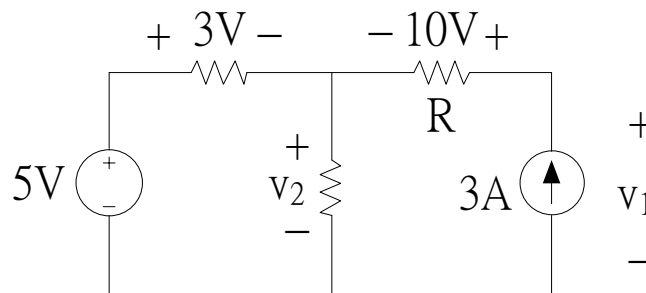


Figure P2.21

Q5. [Modified from Rizzoni Problem 2.49]

For the circuit shown in Figure P2.49, find the equivalent resistance across the terminals. Let $R_1 = 5\ \Omega$, $R_2 = 6\ \Omega$, $R_3 = 4\ \Omega$, $R_4 = 10\ \Omega$, $R_5 = 7\ \Omega$ and $R_6 = 10\ \Omega$.

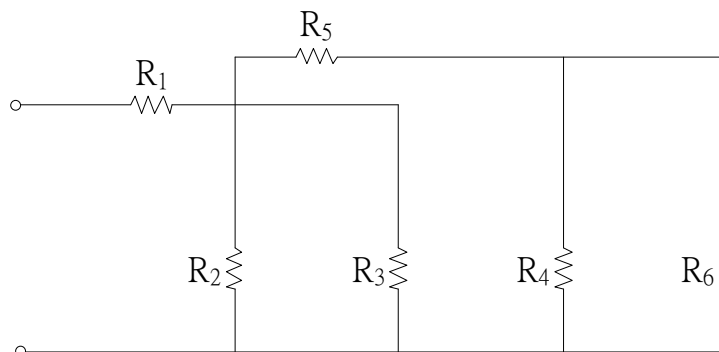


Figure P2.49

Intermediate Level

Q6. [Rizzoni Problem 2.47]

Find the equivalent resistance between terminals a - b in the circuit of Figure P2.47.

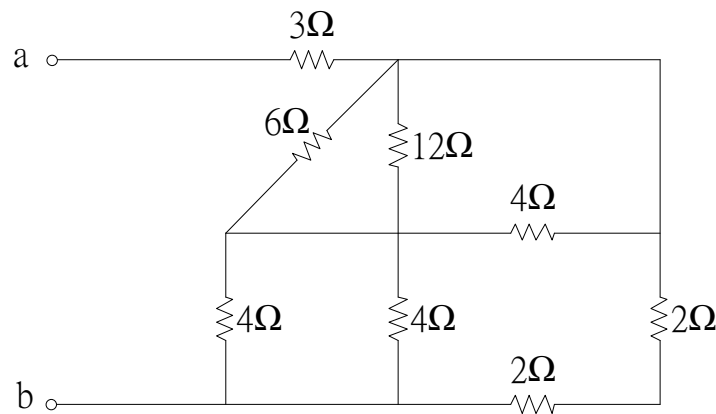


Figure P2.47

Q7. [Rizzoni Problem 2.64]

In the circuit of Figure P2.64, find the equivalent resistance:

- Across a - b when (i) terminals c - d are open and (ii) when terminals c - d are shorted together.
- Across c - d when (i) terminals a - b are open and (ii) when terminals a - b are shorted together.

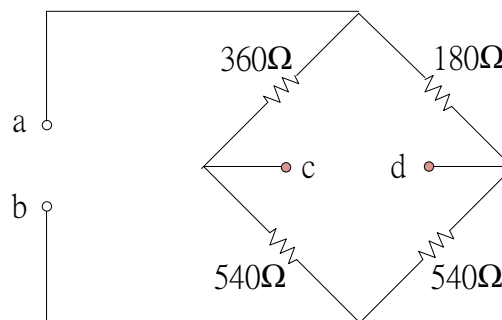


Figure P2.64

Q8. [Alexander Problem 2.18]

Apply KVL and Ohm's law to find I and V_{ab} in the circuit of Fig 2.82.

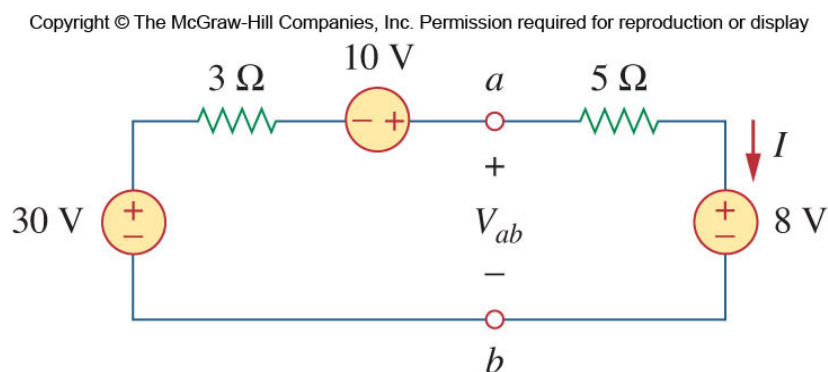


Figure 2.82

Q9. [Rizzoni Problem 2.46]

In the circuit shown in Figure P2.46, the power absorbed by the 15Ω resistor is 15W . Find R . (Hint: Find the voltage across the 15Ω resistor. Then find the equivalent resistance across the terminals of 15Ω . If we denote this resistance by R_{eq} , next use voltage divider rule with R and R_{eq} in series).

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

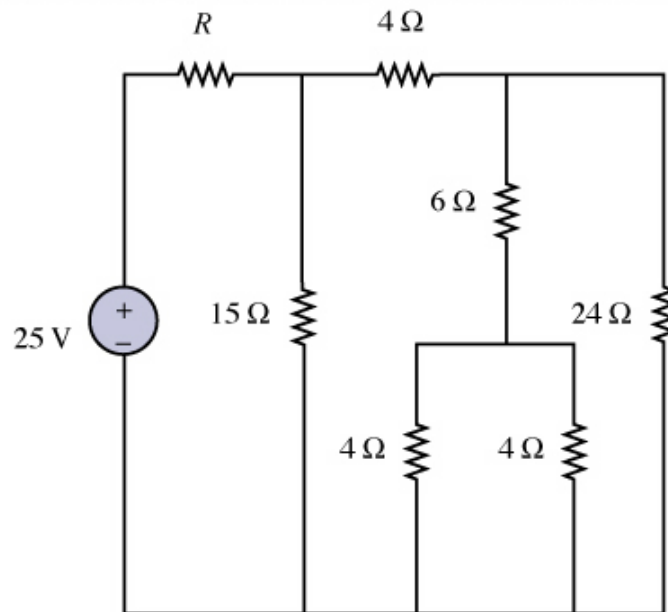


Figure P2.46

Numerical solutions**Q1. [Rizzoni Problem 2.13]**

$$I_2 = 6\text{ A}, I_3 = 2\text{ A}$$

Q2. [Rizzoni Problem 2.24]

$$A = 20\text{ W (dissipating)}, B = 12\text{ W (generating)}, C = 4\text{ W (dissipating)}, D = 12\text{ W (generating)}$$

Q3. [Alexander Problem 2.12]

$$\text{Unknown voltage differences: } v_1 = 70\text{ V}, v_2 = 10\text{ V}, v_3 = 60\text{ V}$$

Q4. [Rizzoni Problem 2.21]

$$\text{Power consumed by resistor R: } 30\text{ W}$$

$$\text{Power supplied by current source: } 36\text{ W}$$

$$\text{Hint: You would need to find } V_1 \text{ and } V_2 \text{ first by applying KVL around any mesh or loop (} V_1 = 12\text{ V, } V_2 = 2\text{ V)}$$

Q5. [Modified from Rizzoni Problem 2.49]

$$7\ \Omega$$

Q6. [Rizzoni Problem 2.47]

$$5\ \Omega$$

Q7. [Rizzoni Problem 2.64]

$$\text{Part (a)(i) } 400\ \Omega$$

$$\text{Part (a)(ii) } 390\ \Omega$$

$$\text{Part (b)(i) } 360\ \Omega$$

$$\text{Part (b)(ii) } 351\ \Omega$$

Q8. [Rizzoni Alexander Problem 2.18]

$$I = 4\text{ A}$$

$$V_{ab} = 28\text{ V}$$

Q9. [Rizzoni Problem 2.46]

$$R = 4\ \Omega$$