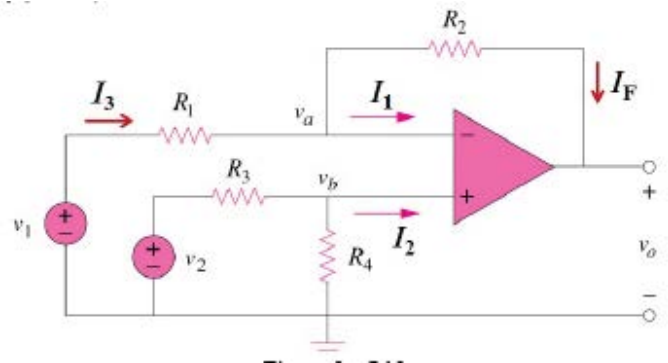


Student ID: _____ Student Name: _____

1) For the circuit in Fig 1, assuming the op amp is ideal, and given that $R_2 = R_4 = 90 \text{ k}\Omega$. $R_1 = R_3 = 10 \text{ k}\Omega$, $v_1 = 1 \text{ V}$ and $v_2 = 2 \text{ V}$,

- Find v_a and v_b ;
- Find I_3 , I_F and v_o .

3 marks**Fig 1**

2) With reference to the circuit in Fig 2, assuming all op amps to be ideal,

4 marks

- Identify the type of amplifier circuit associated with each of the op amps (label next to the op amp);
- Find V_1 , V_2 , V_3 , V_4 , V_5 , and v_o
- Find v_o again if all the $10\text{ k}\Omega$ resistors were reduced to $2\text{ k}\Omega$.

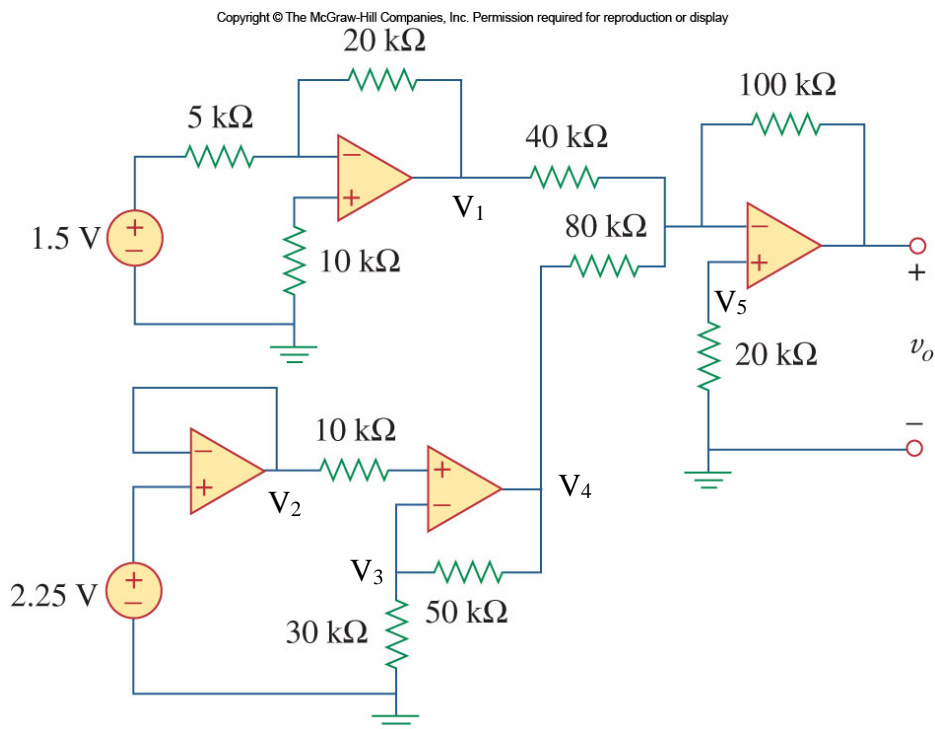


Fig 2

3

3 marks

a) Prove that transfer function of the filter shown in Fig 3 is:

$$\frac{V_o}{V_i} = -\frac{R_f}{R_i} \left(\frac{1}{1 + j\omega C_1 R} \right) \left(\frac{j\omega C_2 R}{1 + j\omega C_2 R} \right)$$

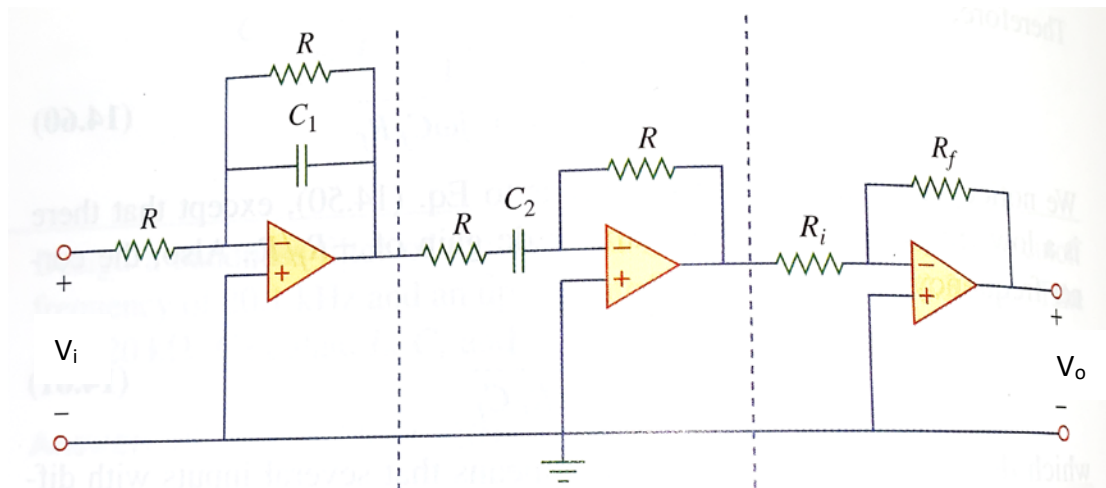


Fig 3

b) Define $\omega_1 = \frac{1}{RC_1}$ and $\omega_2 = \frac{1}{RC_2}$. If $\omega_2 < \omega_1$, is the filter in Fig 3 a low-pass, high-pass, bandpass or bandstop filter?

c) At the center frequency $\omega_o = \sqrt{\omega_1 \omega_2}$, what is the magnitude of the transfer function $\left| \frac{V_o}{V_i} \right|$?