

Review on Ch.4-6 (Part 1)

Ch.4

• Low Pass Filter

$$\frac{V_o}{V_i} = \frac{1}{1 + j\omega/\omega_c} \leftarrow \text{cut-off angular frequency}$$

$A < P^0$


• Range: $f: 0 \rightarrow \infty$

$$|\frac{V_o}{V_i}|: 1 \rightarrow 0$$


$$\angle(\frac{V_o}{V_i}): 0^\circ \rightarrow -90^\circ$$

• Graph:

• Amplitude

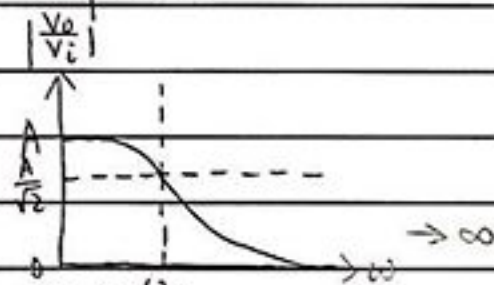

• Phase

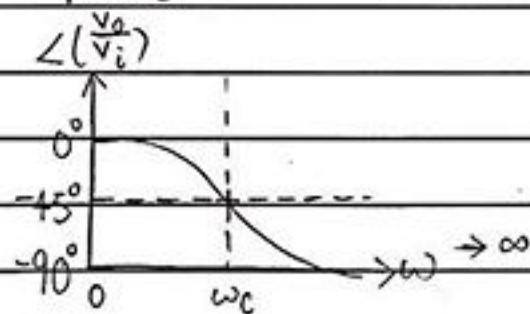

- High Pass Filter

$$V_o = \frac{1}{1 + \omega_c / j\omega}$$

$$V_i = 1 + \omega_c / j\omega$$


- Range: $f: 0 \rightarrow \infty$

$$|\frac{V_o}{V_i}|: 0 \rightarrow 1$$


$$\angle(\frac{V_o}{V_i}): 90^\circ \rightarrow 0^\circ$$

- Graph:

- Amplitude

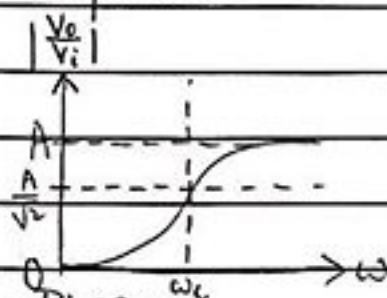

- Phase

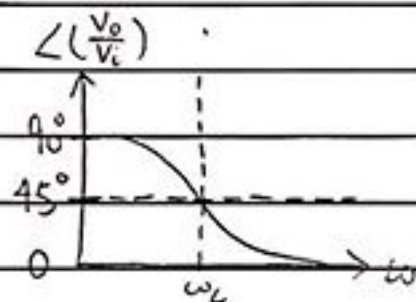

• RCL Series Filter (@Lab)

#cityqueenotes@ig

$$\frac{V_o}{V_i} = \frac{j\omega CR}{1 - \omega^2 LC + j\omega CR}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\sqrt{L/C}}{R}$$


• Range: $\omega: -\infty \rightarrow \omega_0 \rightarrow \infty$

$$\left| \frac{V_o}{V_i} \right|: 0 \rightarrow 1 \rightarrow 0$$


$$\angle \left(\frac{V_o}{V_i} \right): 90^\circ \rightarrow 0 \rightarrow -90^\circ$$

• Graph:

• Amplitude

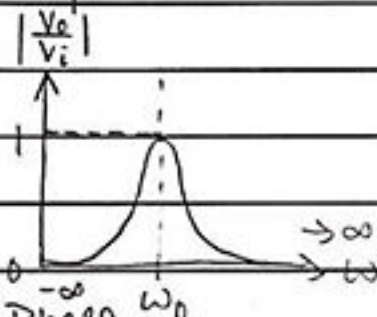

• Phase

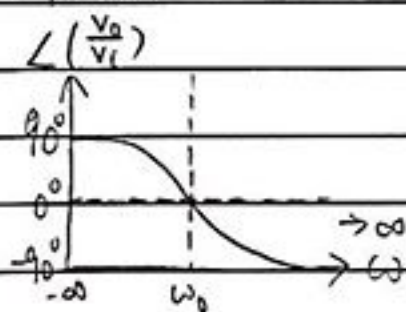

- Ideal Op Amp

- $V^+ = V^-$

- $I_{in} = 0A$


- Open loop gain $A = \infty$

$$V_{out} = A(V_o - V_i)$$

- Input Resistance $R_{in} = \infty$


- Output Resistance $R_{out} = 0$

- Source follower

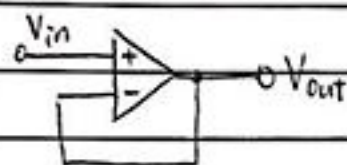

$$\text{Gain} = \frac{V_{out}}{V_{in}} = 1$$

- Inverting amplifier

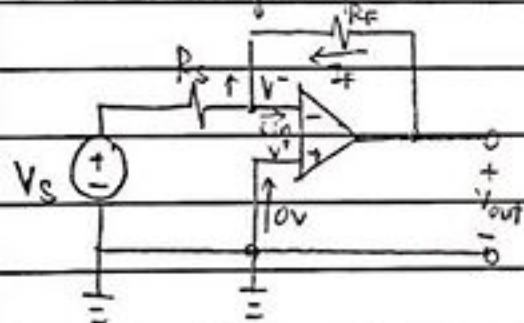

Source $\rightarrow V^-$


Ground $\rightarrow V^+$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -\frac{R_F}{R_S}$$

$$\text{Output Voltage } V_{out} = -V_s \frac{R_F}{R_S}$$

• Non-inverting amplifier

#cityqueenotes @ig

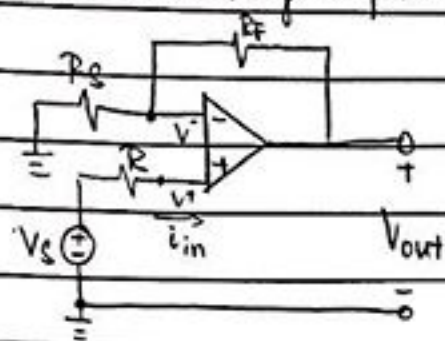


Source $\rightarrow V^+$

Ground $\rightarrow V^-$

$$\text{Gain} = \frac{V_{out}}{V_s} = 1 + \frac{R_F}{R_S}$$

$$\text{Output Voltage } V_{out} = V_s \left(1 + \frac{R_F}{R_S}\right)$$


• Summing amplifier

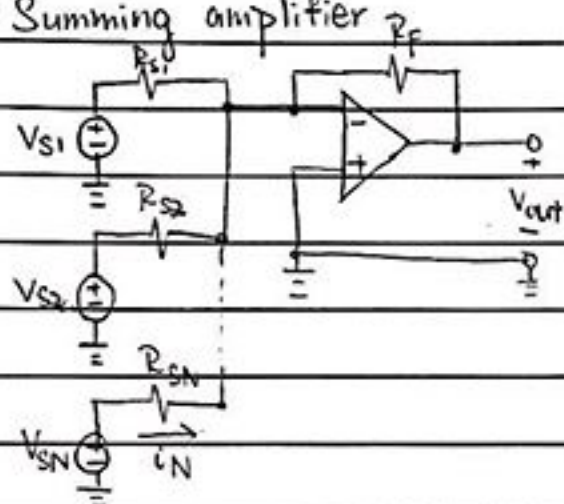

$$\begin{aligned} \text{Output Voltage } V_{out} &= - \left(\frac{R_F}{R_{S1}} V_{S1} + \frac{R_F}{R_{S2}} V_{S2} + \dots + \frac{R_F}{R_{SN}} V_{SN} \right) \\ &= - R_F \left(\frac{V_{S1}}{R_{S1}} + \frac{V_{S2}}{R_{S2}} + \dots + \frac{V_{SN}}{R_{SN}} \right) \end{aligned}$$

• Differential amplifier

#cityueenotes@ig

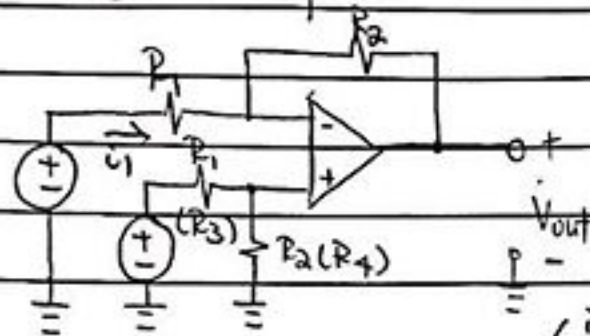

if $(R_1 = R_3 \text{ \& } R_2 = R_4)$

$$\begin{aligned} \text{Output Voltage } V_{out} &= \frac{R_2}{R_1} (V_2 - V_1) \\ &= \frac{R_2 (1 + R_1/R_2)}{R_1 (1 + R_3/R_4)} V_2 - \frac{R_2}{R_1} V_1 \end{aligned}$$


• Cascaded amplifiers

Application of Multiple Types of Amplifiers

Review on Ch.1-6 (Part 2)

Ch.6

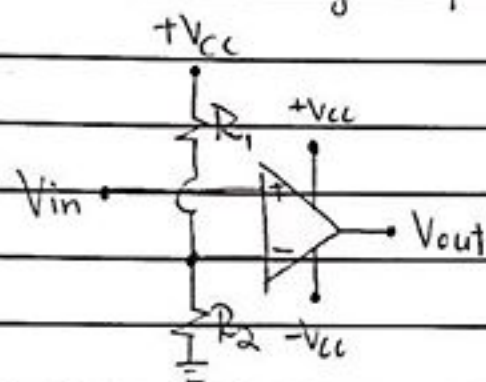
- Op-amp applications
- Non-inverting comparator



$$V_{REF} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_{out} = \begin{cases} +V_{CC} & V_{in} > V_{REF} \\ -V_{CC} & V_{in} < V_{REF} \end{cases}$$


- Inverting comparator

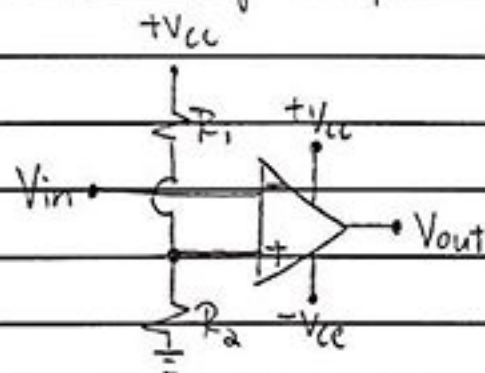

$$V_{out} = \begin{cases} -V_{CC} & V_{in} > V_{REF} \\ +V_{CC} & V_{in} < V_{REF} \end{cases}$$


Real-life Problems

Differential op amp in practice

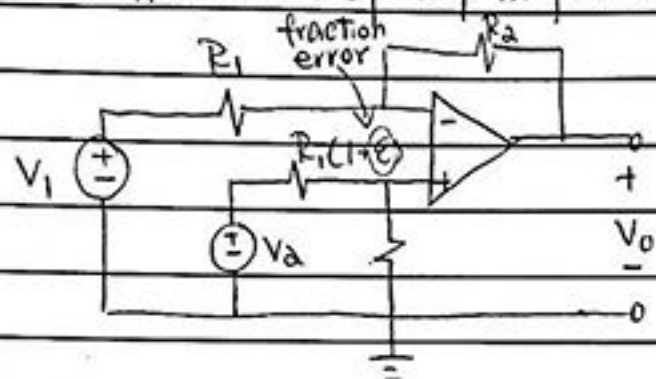


$$V_0 = \frac{R_2}{R_1} (V_2 - V_1) - \frac{\epsilon R_2}{R_1(1+\epsilon) + R_2} V_2$$

Effect of source resistance

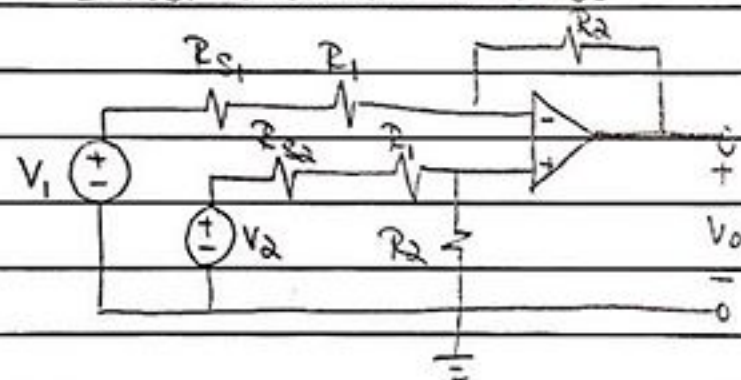


$$V_0 = \left(\frac{R_2}{R_1 + R_{S1}} \right) \left[\left(\frac{R_2 + R_1 + R_{S1}}{R_1 + R_2 + R_{S2}} \right) V_2 - V_1 \right]$$

Instrumentation amplifier

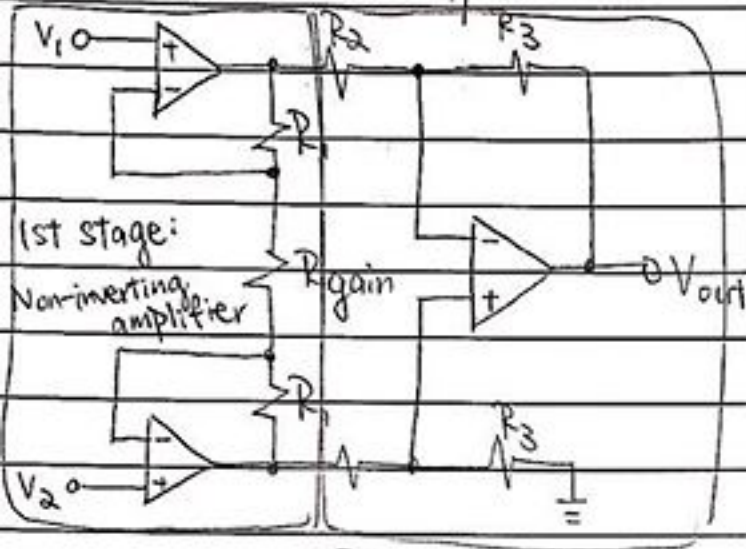


$$V_{out} = \left(1 + \frac{2R_1}{R_{gain}}\right) \left(\frac{R_3}{R_2}\right) (V_2 - V_1)$$

Differentiating amplifier

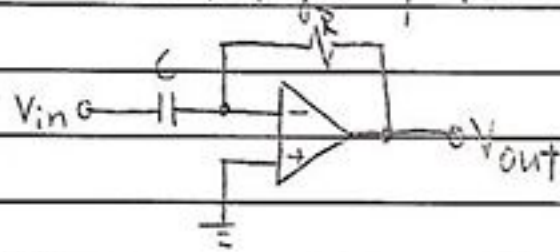

$$V_{out} = -RC \left(\frac{dV_{in}}{dt}\right)$$

Integrating amplifier

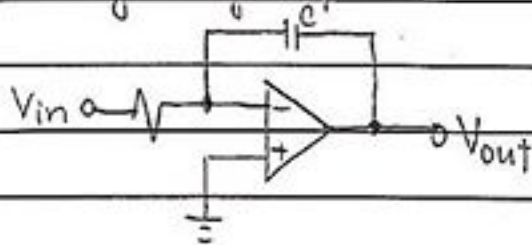

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

Decibels (dB)

#citygreenotes@ig

$$\text{Gain} = 10 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}} \text{ dB}$$

$$= 20 \log_{10} \frac{V_{\text{out}}}{V_{\text{in}}} \text{ dB} \quad (P = \frac{V^2}{R})$$

e.g. Low pass filter: $0 \rightarrow \infty$


$$\text{Gain: } 1 \rightarrow \frac{1}{\sqrt{2}} \rightarrow 0 \quad \omega_c$$

$$0 \text{ dB} \rightarrow -3 \text{ dB} \rightarrow -\infty \text{ dB}$$

$$\text{Factor: } \times 10 \rightarrow +20 \text{ dB}$$

$$\div 10 \rightarrow -20 \text{ dB}$$

Passive 2nd order low pass filter

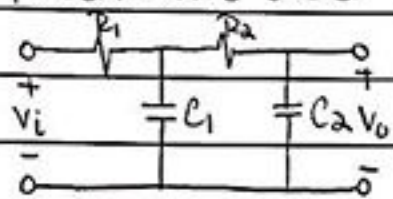


$$\frac{V_o}{V_i}(j\omega) = \left(\frac{1}{1 + j\omega/\omega_{c1}} \right) \left(\frac{1}{1 + j\omega/\omega_{c2}} \right)$$

$$= \frac{1}{[1 + j(\omega/\omega_c)]^2} \quad (\text{if } \omega_{c1} = \omega_{c2} = \omega_c)$$

$$\omega_{c1} = \frac{1}{R_1 C_1} \quad f_{c1} = \frac{\omega_{c1}}{2\pi}$$


$$\omega_{c2} = \frac{1}{R_2 C_2} \quad f_{c2} = \frac{\omega_{c2}}{2\pi}$$
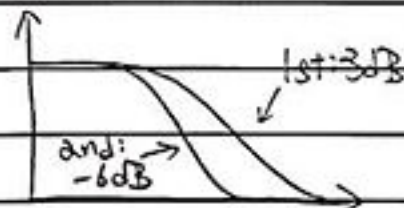
$$\text{Gain: } -3 \text{ dB} \rightarrow -6 \text{ dB}$$



• Active 1st order low pass filter

#cityueenotes@ig

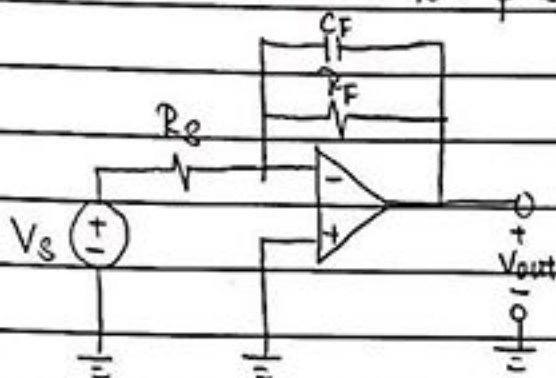


$$\frac{V_{out}}{V_s}(j\omega) = - \frac{(R_F/R_s) \leftarrow G}{1 + j\omega(C_F R_F) \leftarrow \frac{1}{\omega_c}}$$

$$\omega_c = \frac{1}{R_F C_F} \quad f_c = \frac{\omega_c}{2\pi}$$

$$\text{Passband gain } G = \frac{R_F}{R_s}$$

• Active 1st order high pass filter


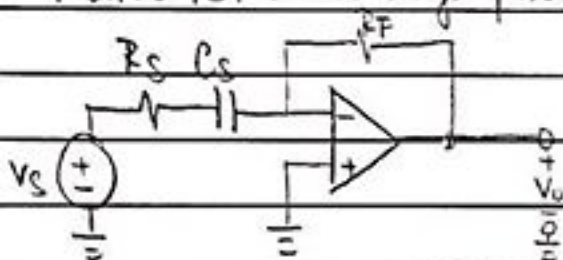


$$\frac{V_{out}}{V_s}(j\omega) = - \frac{(R_F/R_s) \leftarrow G}{1 + (1/j\omega)(C_s R_s) \leftarrow \frac{1}{\omega_c}}$$

$$\omega_c = \frac{1}{R_s C_s} \quad f_c = \frac{\omega_c}{2\pi}$$

$$\text{Passband Gain } G = \frac{R_F}{R_s}$$


• Active Bandpass Filter

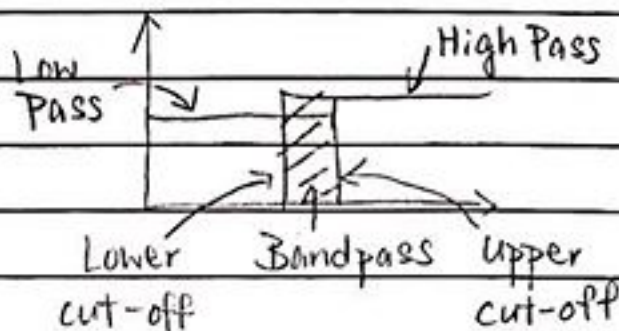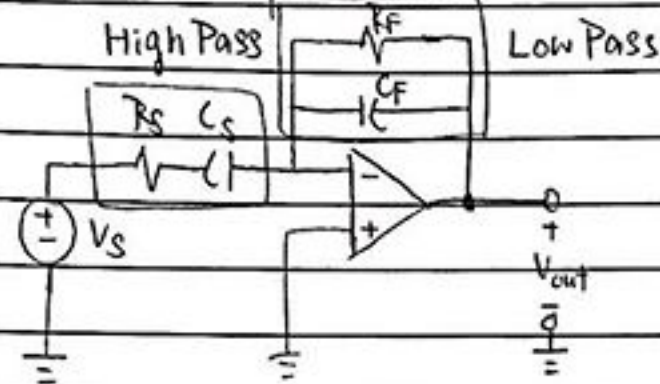

$$\frac{V_{out}}{V_s}(j\omega) = \frac{-R_F/R_s}{(1 + 1/j\omega C_s R_s)(1 + j\omega C_F R_F)}$$

$$= \frac{-R_F/R_s}{(1 + \omega_{HP}/j\omega)(1 + j\omega/\omega_{LP})}$$

- Lower cut-off frequency $\omega_{HP} = \frac{1}{C_s R_s}$ $f_{HP} = \frac{\omega_{HP}}{2\pi}$
- Upper cut-off frequency $\omega_{LP} = \frac{1}{C_F R_F}$ $f_{LP} = \frac{\omega_{LP}}{2\pi}$
- Passband gain $G = \frac{R_F}{R_s}$

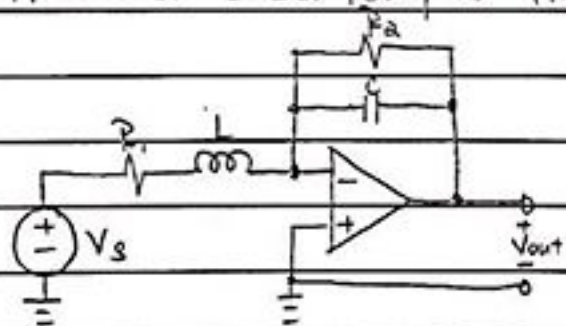• Active 2nd order low pass filter


$$\frac{V_{out}}{V_s}(j\omega) = \frac{-R_2/R_1}{(1 + j\omega C R_2)(1 + j\omega L/R_1)}$$

$$= \frac{-R_2/R_1}{(1 + j\omega/\omega_c)^2} \quad \text{if } \omega_c = \frac{1}{CR_2} = \frac{R_1}{L}$$

Passband Gain $G = \frac{R_2}{R_1} = \frac{R_2}{R_1}$ $f_c = \frac{\omega_c}{2\pi}$

Multiple Feedback Narrow Band Filter

#cityueenotes@ig

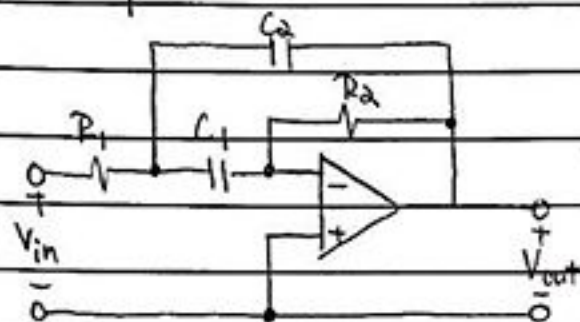

Remarks: Fourier Transform $\rightarrow H(j\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt$

Laplace Transform $\rightarrow H(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{-\frac{1}{R_1 C_2} s}{s^2 + \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2}\right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$

Complex
 $s = \sigma + j\omega$

$$= \frac{\frac{\omega_0}{Q} K s}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2}$$

$$\omega_0 = \frac{1}{C \sqrt{R_1 R_2}} \quad f_0 = \frac{\omega_0}{2\pi}$$


$$Q = \frac{1}{2} \sqrt{\frac{R_2}{R_1}}$$

$$K = -2Q^2$$

$$= -\frac{R_2}{2R_1}$$

Multiple Feedback Narrow Band Filter (General Form)

#cityueenotes@ig

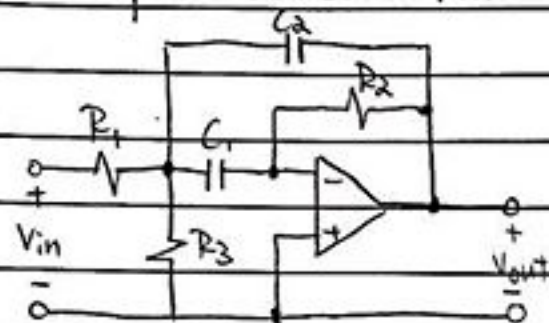

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{-\frac{1}{R_1 C_2} s}{s^2 + \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2}\right) s + \frac{1}{R_2 C_1 C_2} \left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$


$$= \frac{\frac{\omega_0}{Q} K s}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2}$$

$$\omega_0 = \frac{1}{C} \sqrt{\frac{1}{R_2} \left(\frac{1}{R_1} + \frac{1}{R_2}\right)} \quad f_0 = \frac{\omega_0}{2\pi}$$

$$Q = \frac{1}{2} \sqrt{R_2 \left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$

$$K = -\frac{R_2}{2R_1}$$


Sallen-Key Filter Topology

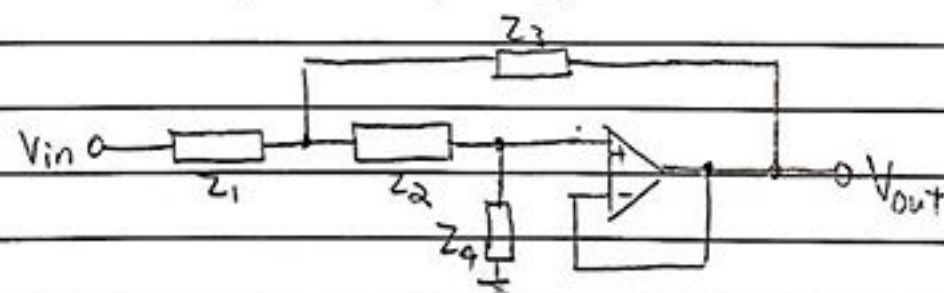

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

• Sallen-Key Filter Topology : Low Pass Filter

#cityneenotes@ig

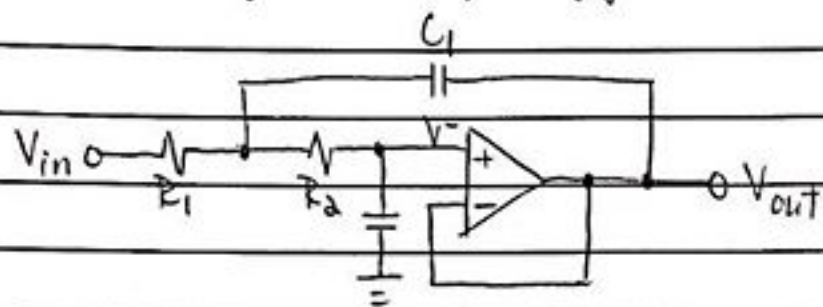


$$H(s) = \frac{\omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad f_0 = \frac{\omega_0}{2\pi}$$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_2 (R_1 + R_2)}$$

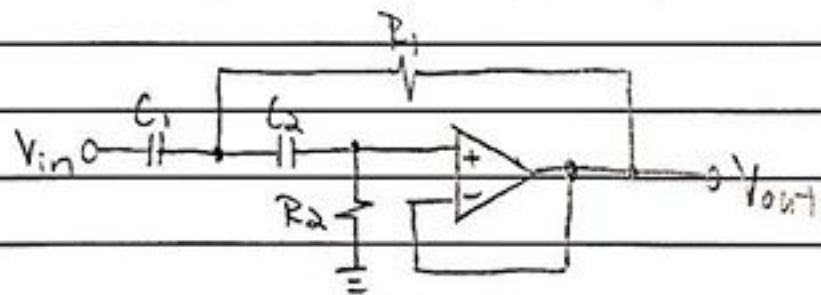• Sallen-Key Filter Topology : High Pass Filter



$$H(s) = \frac{\omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad f_0 = \frac{\omega_0}{2\pi}$$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 (C_1 + C_2)}$$