

1.

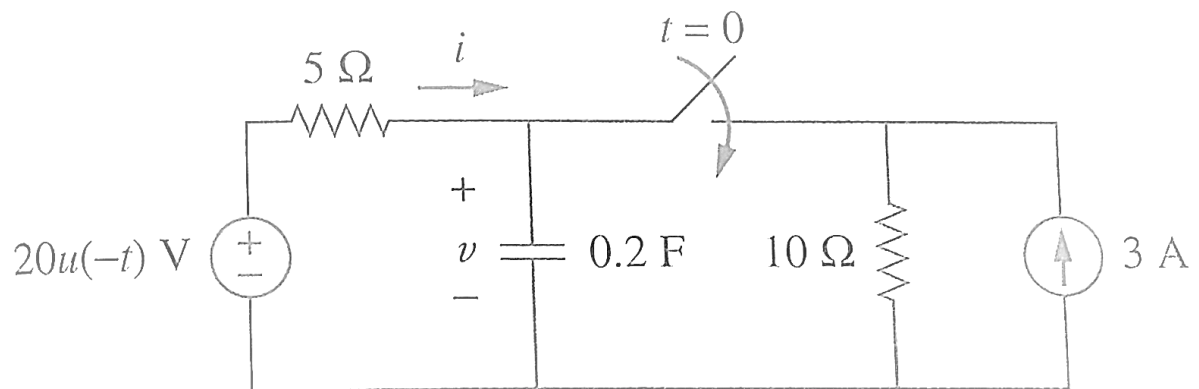


Figure 1

a) In Figure 1, the switch is closed at $t=0$. Note that $u(t)$ is a step function. $u(-t)=1$ for $t<0$ and 0 for $t > 0$. Find $i(t)$ when $t < 0$.

b) For the circuit in Figure 1, find $v(t)$, unit in V, when $t < 0$.

c) For the circuit in Figure 1, find $i(t)$ and $v(t)$ for $t > 0$.

2.

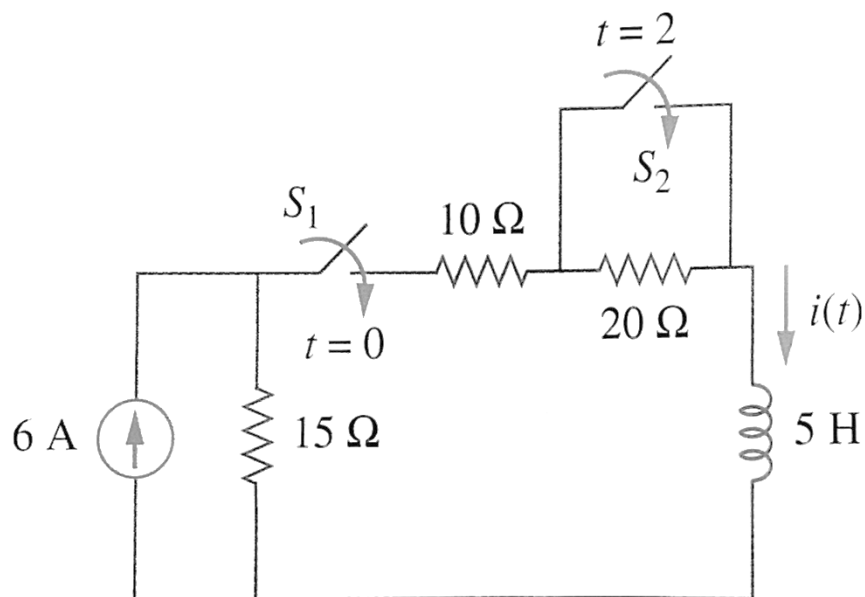


Figure 2

a) In Figure 2, switch S_1 is closed at $t=0$, and switch S_2 is closed at $t=2$ s. Find $i(1)$, in A.

b) For the circuit in Figure 2, find $i(3)$, in A.