

AC Overview

I. Components

- Capacitors (C) [Section 6.2, 6.3]
- Inductors (L) [Section 6.4, 6.5]
- C & L vs. R \rightarrow Storage vs. Dissipation [Section 6.1]

Alexander & Sadiku,
“Fundamentals of Electric Circuits”
5th Edition Chapters 6, 9

II. Concepts

- Sinusoids [Section 9.1, 9.2]
- Phasors (complex numbers) [Section 9.3, 9.4]
- Impedance & Admittance [Section 9.5]




III. Combine and apply

- Apply Kirchhoff's laws in Frequency Domain [Section 9.6]
- Impedance combinations [Section 9.7]

Capacitor and Capacitance

Capacitor

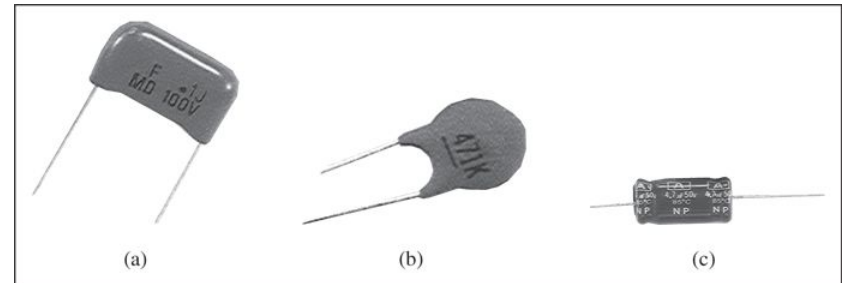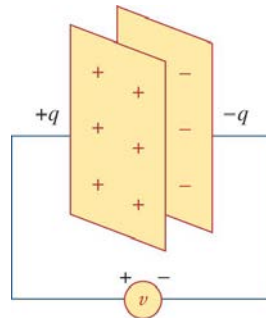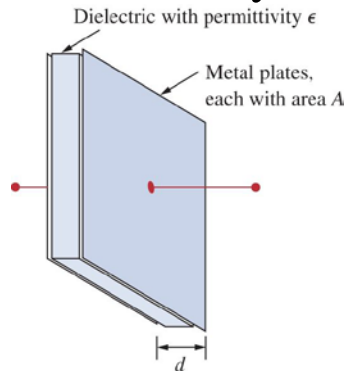- Simplest way to form a capacitor is to sandwich an insulator (technical term is dielectric) between a pair of parallel conducting plates
- Hence the symbol for a capacitor is two parallel lines separated by a gap



$$Q = CV$$

The circuit symbol for a capacitor, consisting of two parallel vertical lines. It is shown in a circuit diagram with a voltage source v connected across it, with the positive terminal on the left and the negative terminal on the right.

Capacitance

- Commonly symbolized by the letter C with unit of Farads (F)
- Relates the amount of charge stored for a given voltage applied
- No energy dissipated unlike resistors
- Energy is stored (in keeping the plates apart)

DC and AC response in Capacitor

$$\begin{array}{c} + \\ V \\ - \end{array} \begin{array}{c} \text{---} \\ \text{---} \\ \text{---} \end{array} \begin{array}{c} \circ \\ \text{---} \\ \circ \end{array} \quad Q(t) = CV(t) \xrightarrow[\text{with respect to time}]{\text{Differentiate}} \boxed{i(t) = C \frac{dV(t)}{dt}}$$

If voltage is constant with time: $dV/dt = 0 \rightarrow I = 0$

No voltage change \rightarrow No current

Case study to consider:

Given that $C = 1 \text{ nF}$

If $V(t) = 1 \sin(10t) \rightarrow Q(t) = \underline{\hspace{2cm}}$

$\rightarrow i(t) = \underline{\hspace{2cm}}$

If voltage changes with time: $dV/dt \neq 0 \rightarrow I \neq 0$

Voltage change \rightarrow Charge changes \rightarrow Current

Summary: Capacitor response to DC & AC

1) If applied voltage is DC

- Insulating dielectric blocks the current from flowing through
- Plates will charge up
- At DC, capacitor blocks current from flowing through




2) If applied voltage is AC (e.g. sinewave)

- Charge on the plates also likewise varies in time with the AC
- Capacitor therefore does not act as an open circuit in the presence of an AC
- In AC, capacitor allows current to pass through


Inductors and Inductance

Inductor

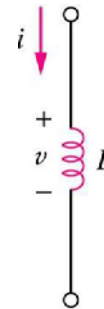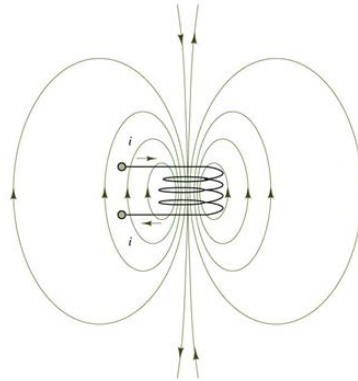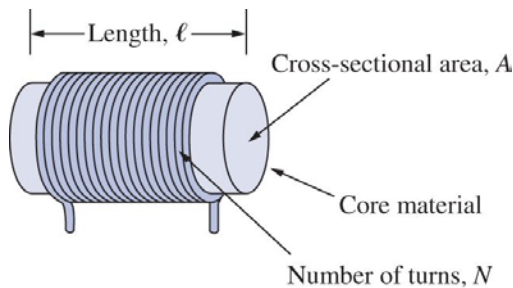- Simplest way to form an inductor is to winding a coil around a core that concentrates magnetic field lines (flux)
- Hence symbol of an inductor is coil between two terminals



$$\phi = Li$$

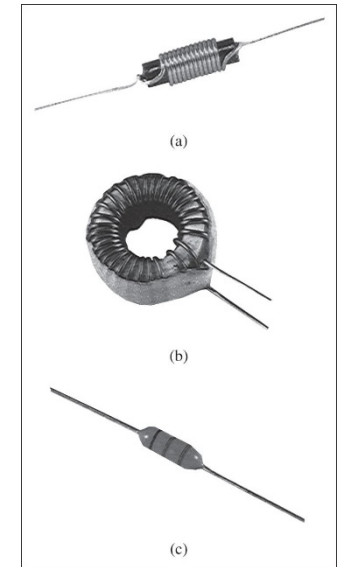


Inductance

- Inductance is commonly symbolized by letter L with unit of Henrys (H)
- Passing a current through an inductor produces a magnetic flux (ϕ) that is related to the inductance (L)
- No energy dissipated unlike resistors (note that wires are assumed to have no resistance by definition)

I-V relation in an inductor

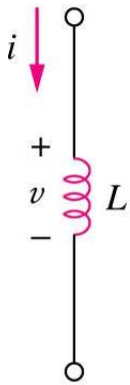If the current through an inductor is time-varying, then the generated voltage must also be time-varying:



$$\text{Flux: } \phi = Li$$

$$\text{Faraday's Law: } v(t) = \frac{d\phi(t)}{dt}$$

$$\text{Differentiating with respect to time (t): } v(t) = L \frac{di(t)}{dt}$$

Voltage depends on the **rate of change** of current

If current is constant with time $\rightarrow di/dt = 0 \rightarrow V = 0$ (No voltage)

No current change \rightarrow No voltage difference

If current changes with time $\rightarrow di/dt \neq 0 \rightarrow V \neq 0$ (There is voltage)

Current change \rightarrow Voltage difference

Sinusoids

Sinusoids can be written as sine or cosine functions

$$x(t) = A \sin(\omega t + \phi)$$

A = amplitude

ω = radian frequency = $2\pi f$ (rad/s)


f = natural frequency (cycles/s or Hz)

T = period = $1/f$ (second)

ϕ = phase (with reference to a cycle: 2π)


We compare the two waves by:

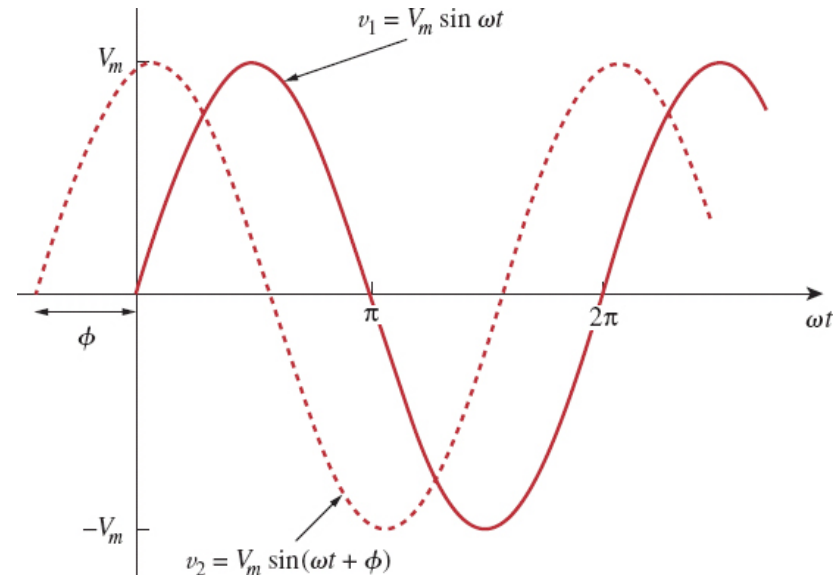- 1) The ratio of their amplitudes
- 2) Phase difference



We can immediately see that an AC signal has as lot more key features than a DC signal. For a DC signal, the magnitude alone is a sufficient quantitative description. But in the case of sinusoidal AC signals, concepts like frequency and phase also need to be considered.

I-V relationship in a resistor

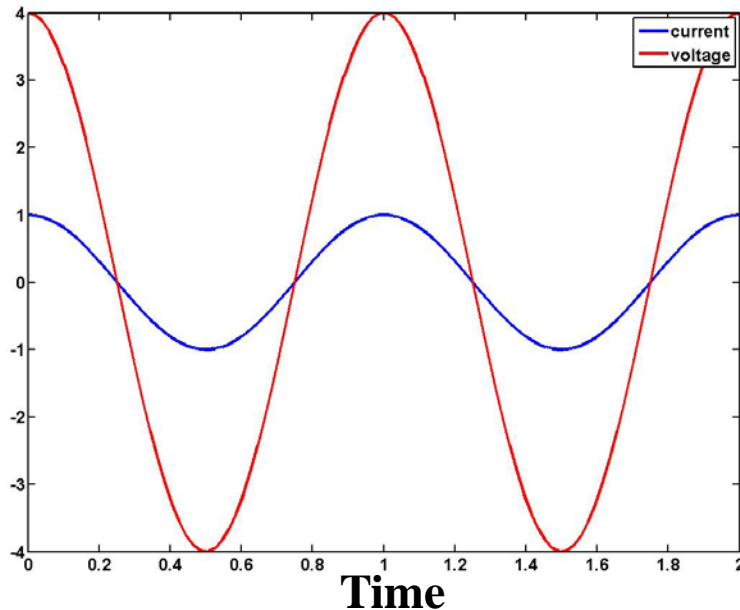


This plot shows the relationship between the current and voltage in a 4Ω resistor when the signal is an AC sinusoid.

It can be seen that there is no phase difference between the voltage and current.

This is because R is simply given by the ratio of voltage to current and there is therefore no phase shift between the two, but simply a scaling in the amplitude.

I-V relationship in a capacitor

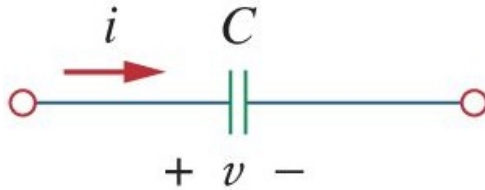

If the voltage across a capacitor is: $V(t) = V_m \cos(\omega t)$

Then the current through it will be:

$$I(t) = C(dV/dt) = -\omega C V_m \sin(\omega t) = \omega C V_m \cos(\omega t + 90^\circ)$$


Shift forward by 90°

Therefore we say that I leads V by 90°

(or $\pi/2$ in radians)


$$\frac{V_m}{I_m} = \frac{1}{\omega C}$$

$$\angle V - \angle I = -\frac{\pi}{2}$$

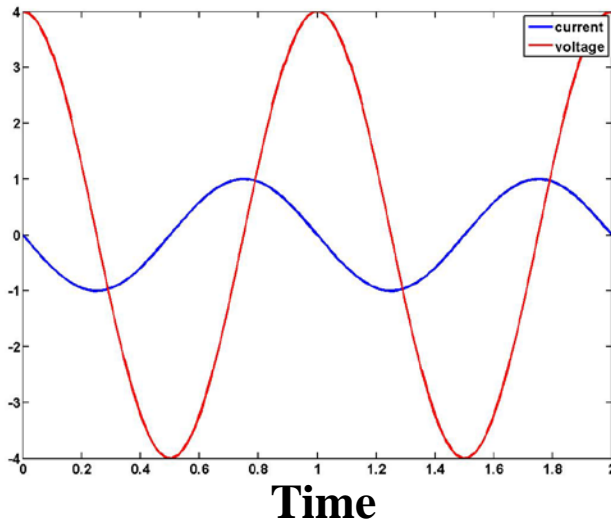

- 1) Current goes through a phase shift relative to the voltage (in a resistor, there is no phase shift between the current and voltage)
- 2) Ratio of voltage to current depends on the capacitance **AND** frequency of the sinusoid (in a resistor, the ratio between voltage and current is simply R and independent of frequency)


I-V relationship in an inductor

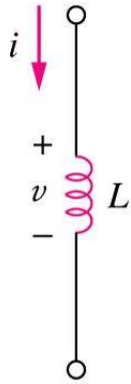

If the current through an inductor is: $i(t) = I_m \cos(\omega t)$

Then the current through it will be:
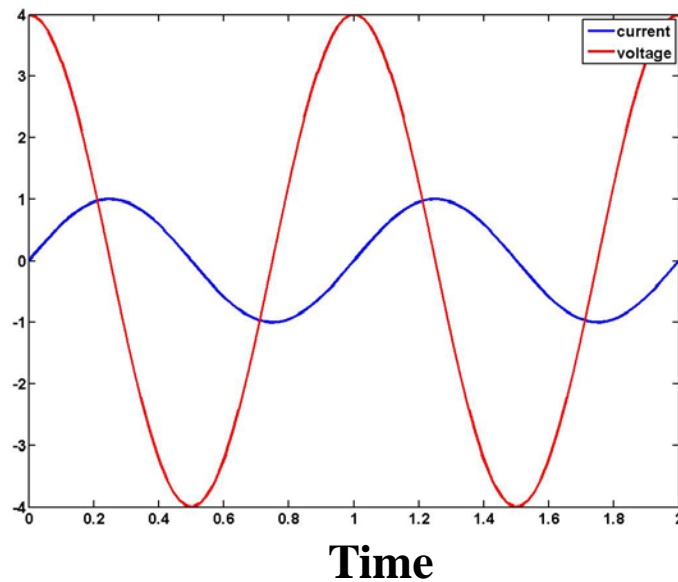
$$v(t) = L(di/dt) = -\omega L I_m \sin(\omega t) = \omega L I_m \cos(\omega t + 90^\circ)$$



Shift forward by 90°

Therefore we say that I lags V by 90°
(or $\pi/2$ in radians)


$$\frac{V_m}{I_m} = \omega L \quad \angle V - \angle I = +\frac{\pi}{2}$$

- 1) Current goes through a phase shift relative to the voltage
- 2) Ratio of voltage to current depends on inductance AND frequency of the sinusoid

Graphical methods


Calculate the phase angle between:
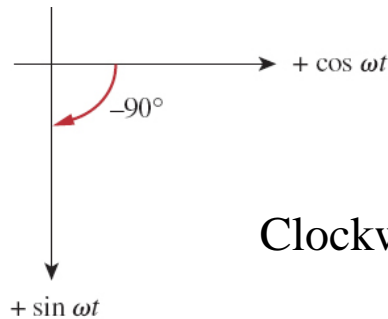
$$v_1 = -10 \cos(\omega t + 50^\circ) \text{ and } v_2 = 12 \sin(\omega t - 10^\circ)$$



(a)


Clockwise: Phase goes backward (-ve)

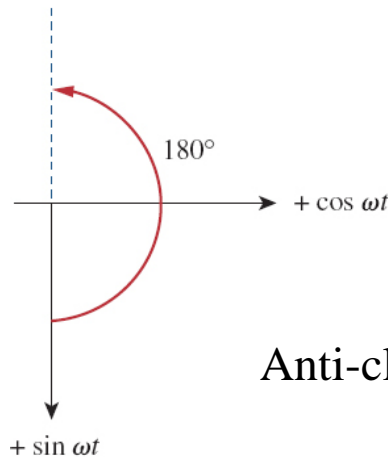

(b)

Anti-clockwise: Phase goes forward (+ve)


$$\angle v_1 - \angle v_2 = -30^\circ$$

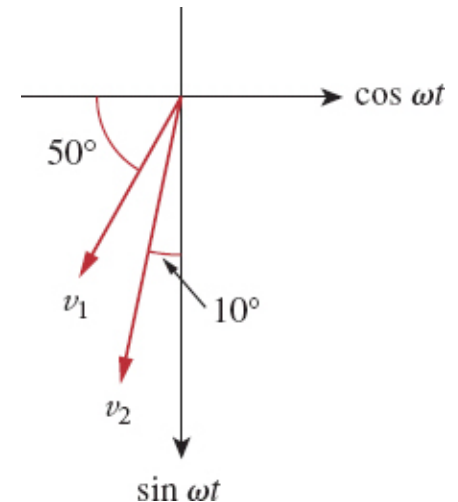

Phasors

- A phasor is a complex number that represents the amplitude and phase of a sinusoid
- Phasors are more convenient to work with than sine and cosine functions and are a powerful tool for analyzing circuits

Imaginary axis

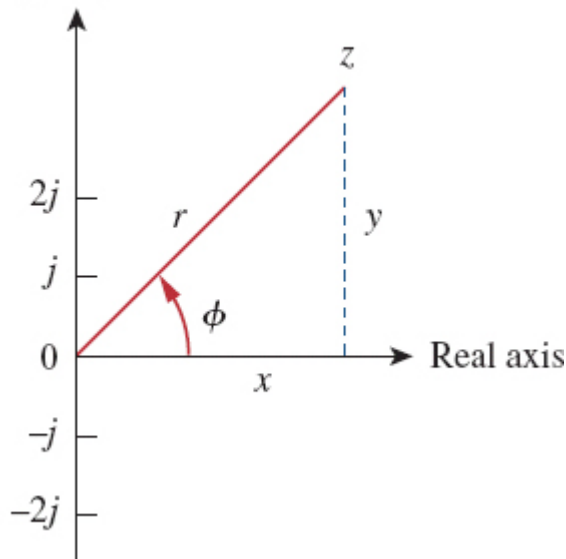

A complex number z can be expressed in **rectangular form** as:

$$z = x + jy$$

Imaginary unit: $j = \sqrt{-1}$

x : real part $\rightarrow \text{Re}(z) = x$; y : imaginary part $\rightarrow \text{Im}(z) = y$

The complex number z can be expressed in **polar form** or **exponential form** as:

$$z = r \angle \phi = r e^{j\phi}$$

$$r = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1} \frac{y}{x}$$

$$x = r \cos \phi \quad y = r \sin \phi$$

Euler's identity

$$e^{+j\phi} = \cos \phi + j \sin \phi$$

Complex number arithmetic

The following mathematical operations are important.

Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication

$$z_1 z_2 = r_1 r_2 \angle (\phi_1 + \phi_2)$$

Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle (\phi_1 - \phi_2)$$

Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle (-\phi)$$

Square Root

$$\sqrt{z} = \sqrt{r} \angle (\phi/2)$$

Complex Conjugate

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

Phasors

A phasor represents a sinusoid as the real component of a vector in the complex plane representation based on Euler's identity:

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

$$\cos \phi = \operatorname{Re}(e^{j\phi}) \quad \sin \phi = \operatorname{Im}(e^{j\phi})$$

Given a sinusoid: $v(t) = V_m \cos(\omega t + \phi)$


$$v(t) = \operatorname{Re}(V_m e^{j(\omega t + \phi)}) = \operatorname{Re}(V_m e^{j\omega t} e^{j\phi})$$

$$v(t) = \operatorname{Re}(V_m e^{j\phi} e^{j\omega t}) = \operatorname{Re}(V e^{j\omega t})$$

, where $V = V_m e^{j\phi} = V_m \angle \phi$

The **length** of the vector is the **amplitude** of the sinusoid.

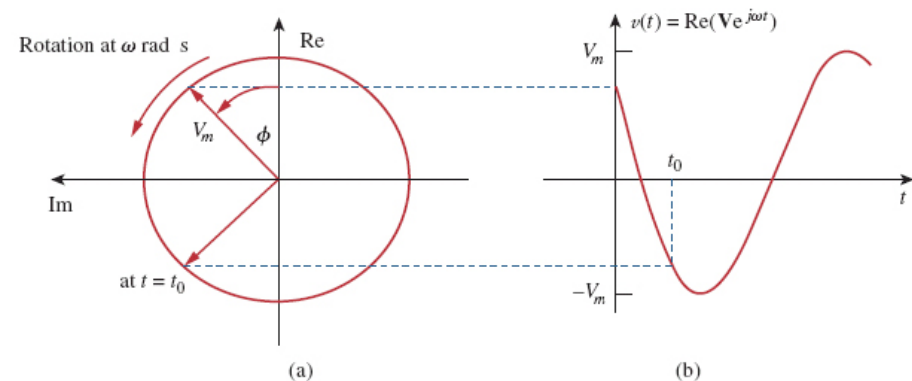The **angle** ϕ of the vector with respect to the positive real axis is the **phase**.



$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow V = V_m \angle \phi$$

(Time-domain
representation)

(Phasor-domain
representation)

Sinusoid-phase transformation


TABLE 9.1

Sinusoid-phasor transformation.

Time domain representation	Phasor domain representation
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	$I_m \angle \theta$
$I_m \sin(\omega t + \theta)$	$I_m \angle \theta - 90^\circ$

Applying a *derivative* to a phasor yields:

$$\frac{dv}{dt} \Rightarrow j\omega V$$

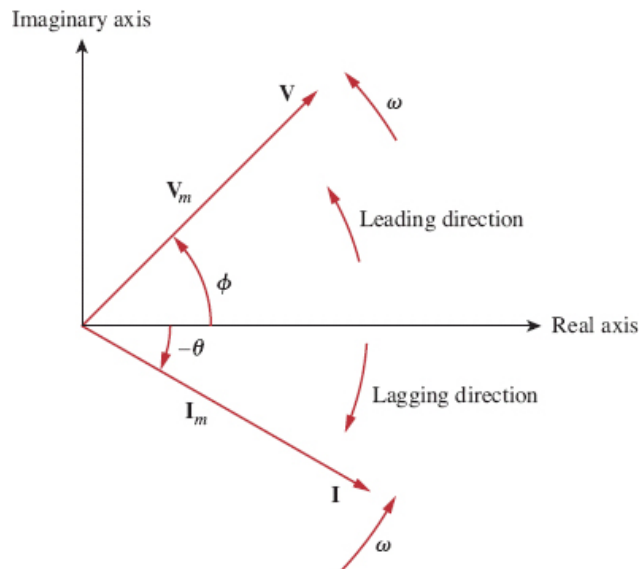


Differences between $v(t)$ and \mathbf{V} to keep in mind:

- 1) $v(t)$ is the time domain form, while \mathbf{V} is the frequency domain form
- 2) $v(t)$ is therefore time-dependent, while \mathbf{V} is not
- 3) $v(t)$ is always real, while \mathbf{V} is general complex

The meaning of “j”


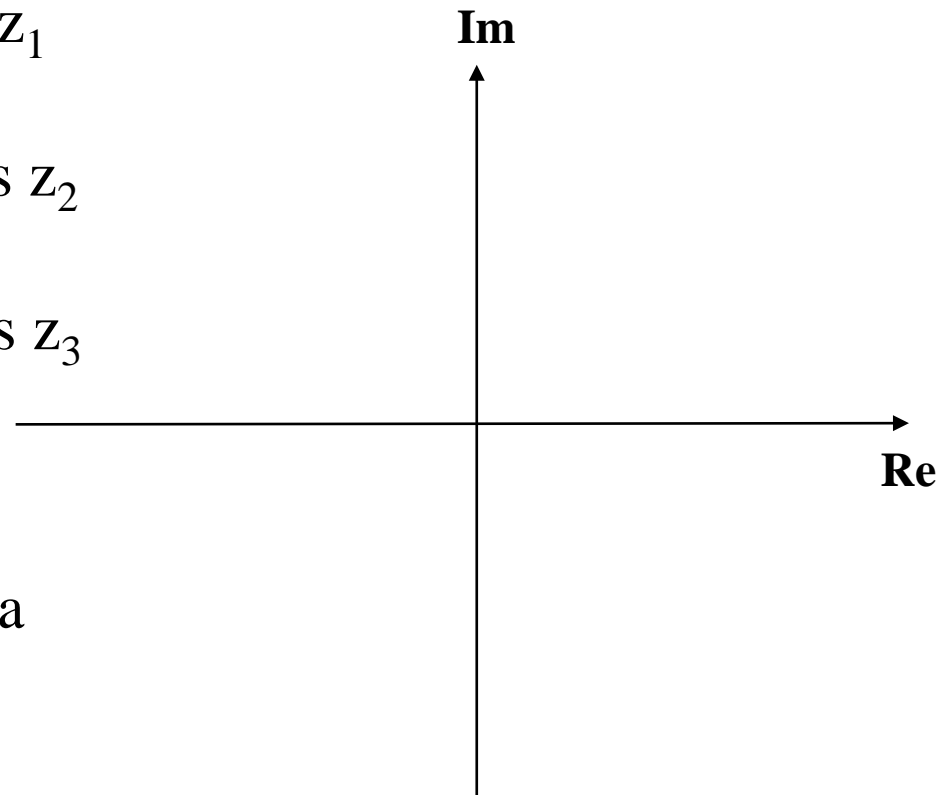
- 1) Draw $z = 3$ on the Im-Re graph
- 2) Multiply z by j , name this as z_1 and draw it on the graph
- 3) Multiply z by $-j$, name this as z_2 and draw it on the graph
- 4) Multiply z by -1 , name this as z_3 and draw it on the graph



What is the effect of multiplying a number by j , $-j$, or -1 ?



Phasor Relationships for Resistors

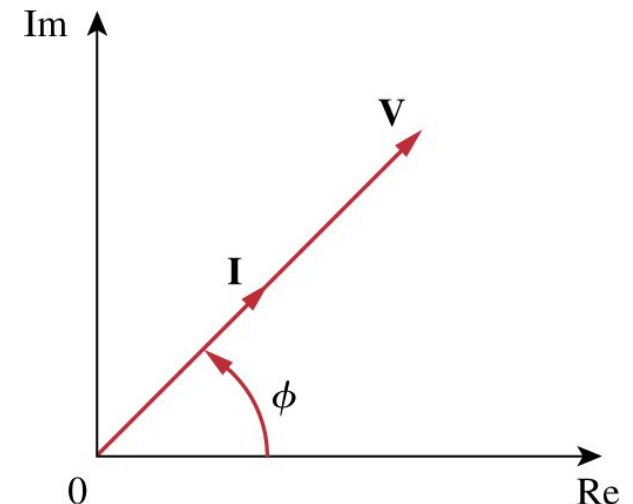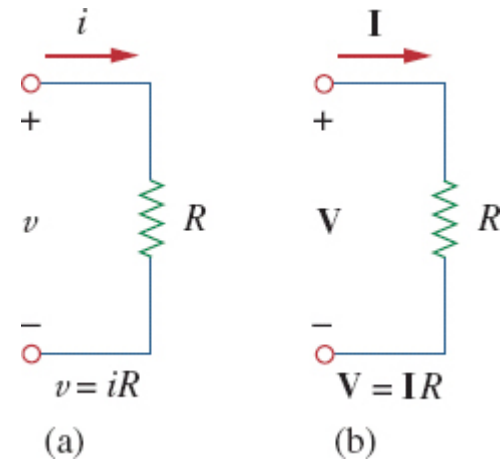- 1) Each circuit element has a relationship between its current and voltage.
- 2) These can be mapped into phasor relationships very simply for resistors capacitors and inductor.
- 3) For the resistor, the voltage and current are related via Ohm's law.
- 4) As such, the voltage and current are in phase with each other.





Phasor Relationships for Inductors

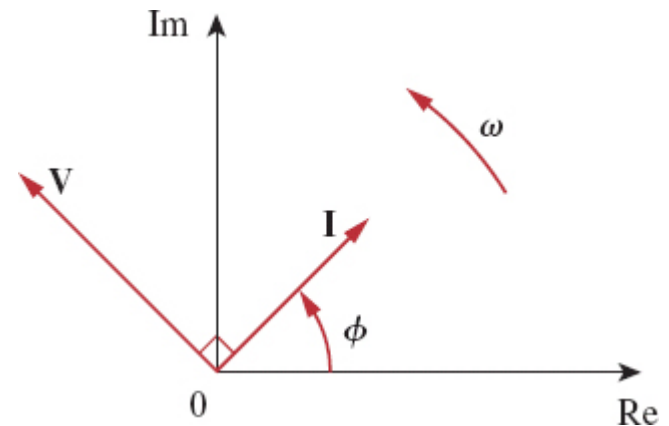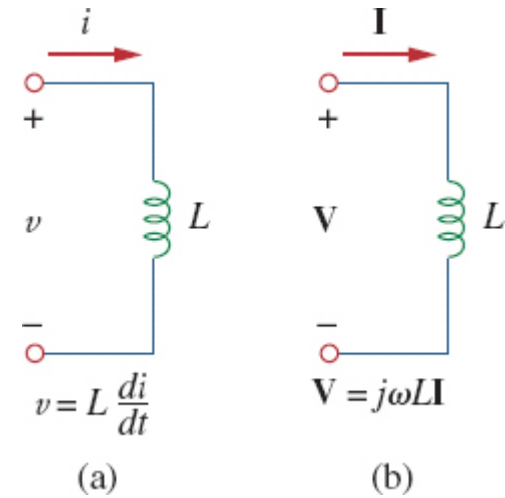- 1) Inductors on the other hand have a phase shift between the voltage and current.
- 2) In this case, the voltage leads the current by 90° .
- 3) Or one says the current lags the voltage, which is the standard convention.
- 4) This is represented on the phasor diagram by a positive phase angle between the voltage and current.



Phasor Relationships for Capacitors

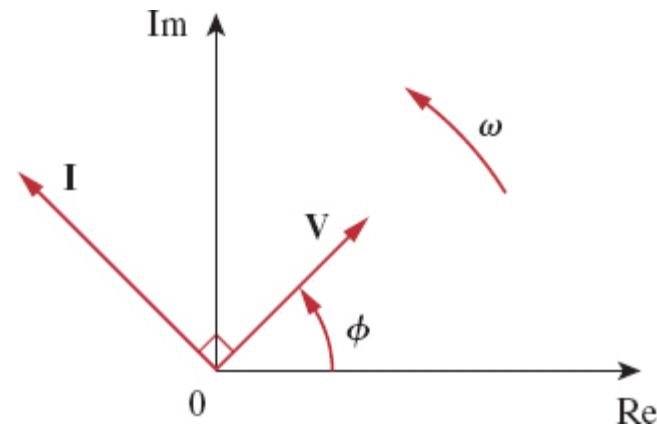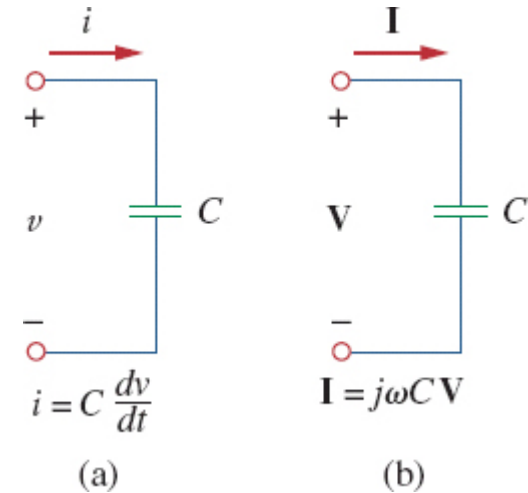- 1) Capacitors have the opposite phase relationship as compared to inductors.
- 2) In their case, the current leads the voltage.
- 3) In a phasor diagram, this corresponds to a negative phase angle between the voltage and current.



Voltage current relationships

TABLE 9.2

Summary of voltage-current relationships.

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Impedance and Admittance

We can now expand Ohm's law to capacitors and inductors. This would have been otherwise tricky as the ratios of voltage and current always changing when working in the time-domain form. In frequency domain it is straightforward.

The impedance of a circuit element is the ratio of the phasor voltage to the phasor current, commonly represented by Z .

$$Z = \frac{V}{I} \quad \text{or} \quad V = ZI \quad \text{Admittance is simply the inverse of impedance: } Y = 1/Z$$

Impedance and Admittance

- In the frequency domain, the values obtained for impedance are only valid at that frequency.
- Changing to a new frequency will require recalculating the values.
- The impedance of capacitors and inductors are shown here:

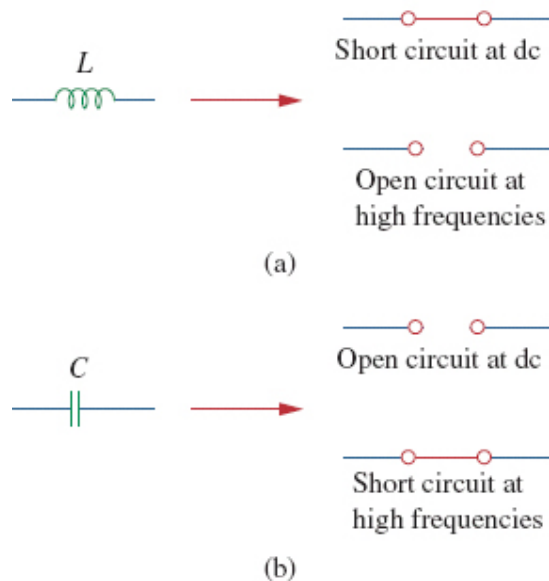


TABLE 9.3


Impedances and admittances of passive elements.

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

Applying Kirchhoff's in frequency domain


Phasors allow Kirchhoff's laws to be applicable. Therefore a circuit transformed to the frequency domain can be evaluated by the same methods developed for KVL and KCL.

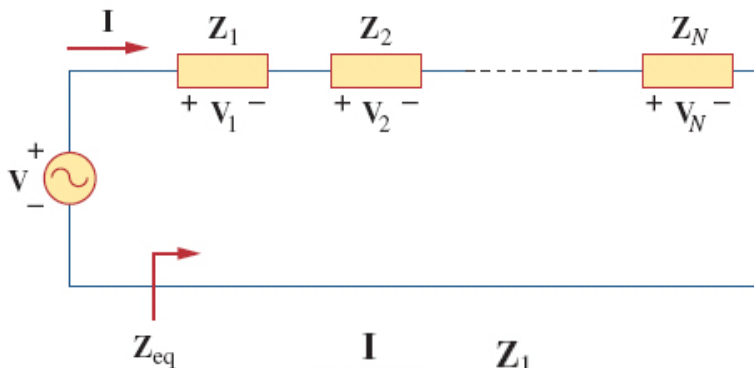Once in the frequency domain, the impedance elements can be combined using the rules for resistors.



Series combinations will result in a sum of the impedance elements:
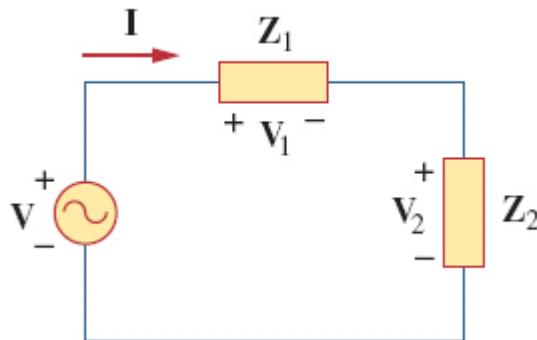
$$Z_{eq} = Z_1 + Z_2 + Z_3 + \cdots + Z_N$$




Elements in series can act like a voltage divider:

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

Parallel combination

Elements combined in parallel will combine in the same fashion as resistors in parallel:
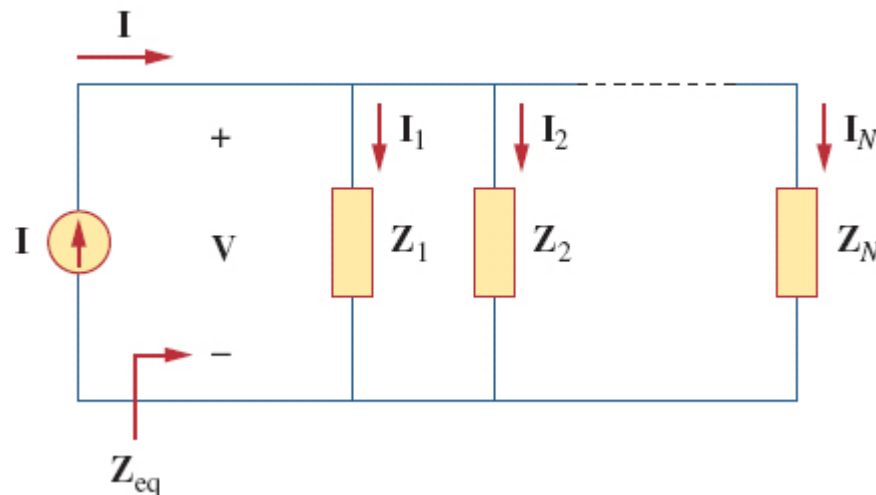
$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \cdots + \frac{1}{Z_N}$$



Expressed as admittance, they are again a sum:

$$Y_{eq} = Y_1 + Y_2 + Y_3 + \cdots + Y_N$$


Impedance: Example 1

Problem 4.61

Work out the impedance (Z) seen across the terminals

When (i) $\omega = 4$ rad/s, (ii) $\omega = 8$ rad/s

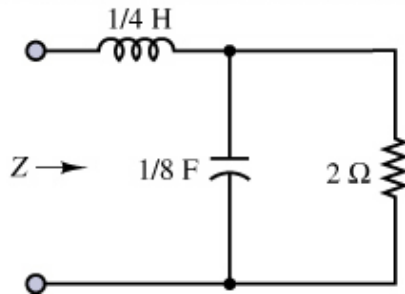Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(i) At 4 rad/s:

Impedance of L:

$$X_L = j\omega L = j(4)(1/4) = j$$

Impedance of C:

$$X_C = 1/j\omega C = 1/[j(4)(1/8)] = -j2$$

Impedance: Example 1 (i) 4 rad/s

When $\omega = 4 \text{ rad/s}$: $X_L = j\omega L = j$; $X_C = 1/j\omega C = -j2$

Impedance of C and parallel with R:

$$\begin{aligned} Z_{RC} &= \frac{X_C R}{R + X_C} = \frac{(-j2)(2)}{2 - j2} = -\frac{j2(1 + j)}{(1 - j)(1 + j)} = -\frac{j2(1 + j)}{2} \\ &= 1 - j \end{aligned}$$

Z_{RC} is in series with impedance of L: $Z = Z_{RC} + X_L$

$$\begin{aligned} &= 1 - j + j \\ &= 1\Omega \end{aligned}$$

Impedance: Example 1 (ii) 8 rad/s

When $\omega = 8 \text{ rad/s}$:

$$X_L = j\omega L = j(8)(1/4) = j2;$$

$$X_C = 1/j\omega C = -j/[(8)(1/8)] = -j$$

Impedance of C and parallel with R: $Z_{RC} = \frac{X_C R}{R + X_C} = \frac{(-j)(2)}{2 - j}$

$$= \frac{-j2(2 + j)}{(2 - j)(2 + j)} = \frac{2}{5}(1 - j2)$$

Z_{RC} is in series with impedance of L: $Z = Z_{RC} + X_L$

$$= \frac{2}{5}(1 - j2) + j2$$
$$= 0.4 + j1.2$$


Impedance depends on the frequency

Impedance: Example 2

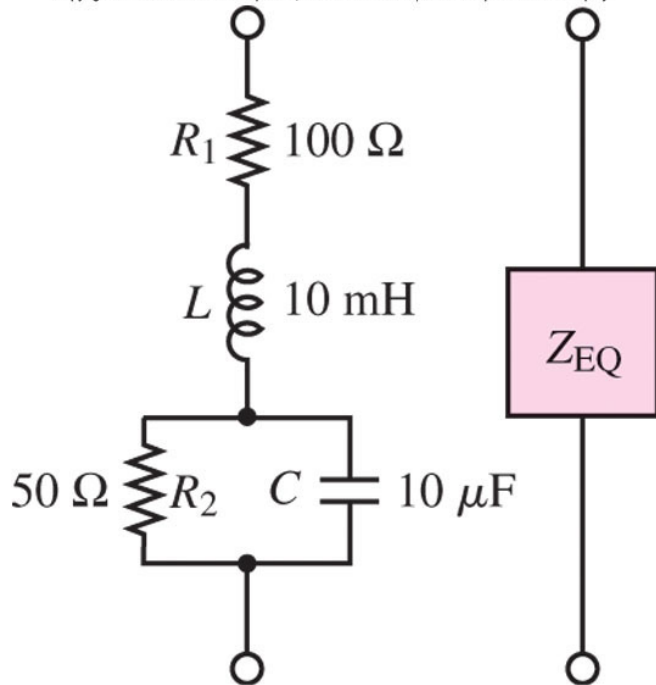Example 4.14 of Rizzoni

Find the equivalent impedance (Z_{EQ}) and admittance (Y_{EQ}) seen across the terminals

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Impedance of L:

$$X_L = j\omega L = j(10^4)(10^{-2}) = j100$$

Impedance of C:

$$X_C = 1/j\omega C = 1/[j(10^4)(10^{-5})] = -j10$$

Given: $\omega = 10^4$ rad/s

Impedance: Example 2 Solution

Impedance of C parallel R_2 :

$$\begin{aligned}Z_{RC} &= \frac{X_C R}{R + X_C} \\&= \frac{(-j10)(50)}{50 - j10} \\&= \frac{500}{10 + j50} \\&= \frac{50}{1 + j5}\end{aligned}$$

Impedance of L series R_1 :

$$\begin{aligned}Z_{RL} &= X_L + R \\&= 100 + j100 \\&= 100(1 + j)\end{aligned}$$

$$\begin{aligned}Z_{EQ} &= Z_{RC} + Z_{RL} \\&= \frac{50}{1 + j5} + 100(1 + j) \\&= 101.92 + j90.385 \\&= 136.2 \angle 41.57^\circ \Omega\end{aligned}$$

$$\begin{aligned}Y_{EQ} &= 1/Z_{EQ} = (1/136.2) \angle -41.6^\circ S \\&= 7.342 \angle -41.6^\circ mS\end{aligned}$$

Admittance

Admittance is simply the **inverse** of the **impedance**: $Y = 1/Z$

Admittance likewise comprises both real and imaginary parts

$$Y = G + jB$$

Real part is called the **AC conductance**

Imaginary part is called the **susceptance**

$$Y = \frac{1}{Z} = \frac{1}{R + jX} = \frac{1}{R + jX} \left(\frac{R - jX}{R - jX} \right) \\ = \frac{R - jX}{R^2 + X^2}$$

$$G = \frac{R}{R^2 + X^2}$$

$$B = -\frac{X}{R^2 + X^2}$$

Example on Admittance



$$Z_{ab} = R_1 + j\omega L$$

$$Y_{ab} = 1/Z_{ab} = 1/(R_1 + j\omega L)$$

$$Y_{ab} = \frac{R_1}{R_1^2 + (\omega L)^2} - \frac{j\omega L}{R_1^2 + (\omega L)^2}$$

$$Y_{ab} = 1/Z_{ab} = 1/R_2 + j\omega C$$

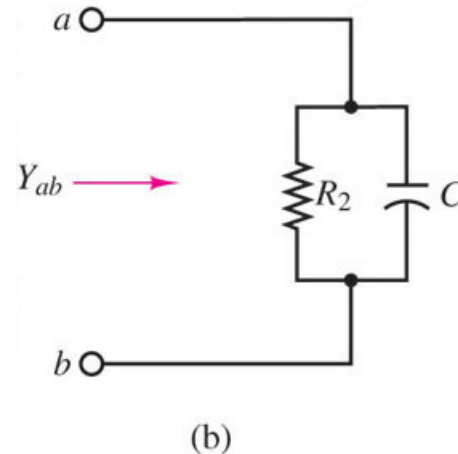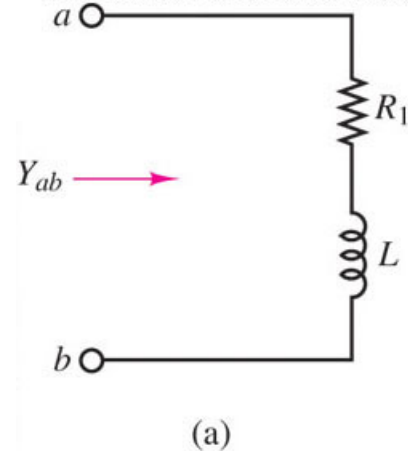Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Summary

- 1) Capacitors: Passes current at high frequency but blocks at DC
- 2) Inductor: Acts as short circuit at DC but blocks current at high frequency
- 3) Impedance introduced as a more general form to describe V/I (magnitude & phase)
- 4) Impedance depends on frequency
- 5) Represent these as phasors so we can add up impedances just like resistances in DC

AC Circuit Analysis

1) Analysis with single source

- Methodology [Section 10.1]
- Two examples

Alexander & Sadiku,
“Fundamentals of Electric Circuits”
5th Edition Chapters 9 &10

2) Analysis with multiple sources (single frequency)

- Nodal analysis [Section 10.2] (1 example)
- Mesh analysis [Section 10.3] (1 example)

3) Analysis by superposition (multiple frequencies)

- Circuits containing DC sources and AC sources of a single frequency (1 example)
- Circuits containing multiple AC sources with different frequencies (1 example)

4) AC Power: Instantaneous vs. Average

General methodology

- 1) Transform the circuit to the frequency domain
 - Transform AC sources from time domain sinusoids to phasor form
 - Work out impedances for a given frequency ω
- 2) Solve the problem using circuit techniques
- 3) Transform phasor form solutions back to time domain

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow V = V_m \angle \phi$$

(Time-domain representation) (Phasor-domain representation)

TABLE 9.3


Impedances and admittances of passive elements.

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

1A) Single source analysis example 1

Alexander 9.50

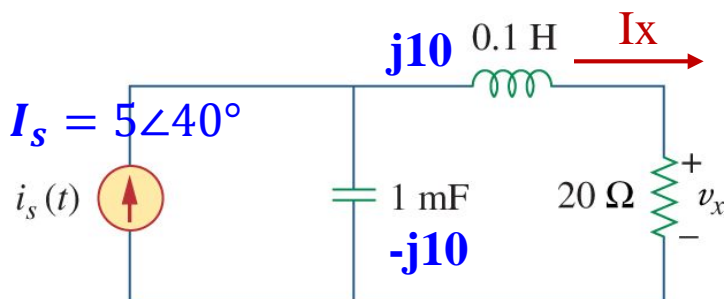Given that $i_s(t) = 5 \cos(100t + 40^\circ)$, determine $v_x(t)$



Step 1a: Transform source to phasor

$$i_s(t) = 5 \cos(100t + 40^\circ) \rightarrow I_s = 5 \angle 40^\circ, \omega = 100 \frac{\text{rad}}{\text{s}}$$

Step 1b: Work out the impedance values

$$1 \text{ mF} \rightarrow -j/(100 * 0.001) = -j10$$

$$0.1 \text{ H} \rightarrow j100 * 0.1 = j10$$

Step 2: Solve using circuit analysis methods

Using current divider rule,

$$I_x = \left(\frac{-j10}{-j10 + j10 + 20} \right) (5 \angle 40^\circ) = (-j0.5)(5 \angle 40^\circ) = 2.5 \angle -50^\circ$$

$$V_x = 20 I_x = 50 \angle -50^\circ$$


Step 3: Transform back to time domain

$$V_x = 50 \angle -50^\circ, \omega = 100 \frac{\text{rad}}{\text{s}} \rightarrow v_x(t) = 50 \cos(100t - 50^\circ) \text{ V}$$

1B) Single source analysis example 2

Alexander 9.42

Determine $v_o(t)$

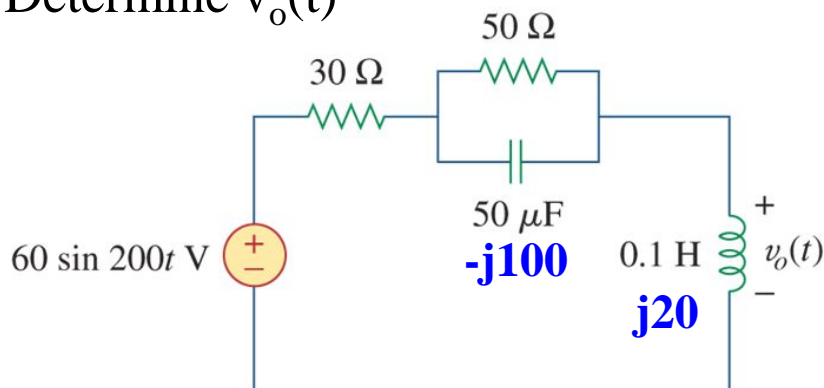

Step 1a: Transform source to phasor

$$60 \sin(200t) \rightarrow 60 \angle -90^\circ, \omega = 200 \frac{\text{rad}}{\text{s}}$$

$$60 \cos(200t - 90^\circ)$$

Step 1b: Work out the impedance values

$$50 \mu\text{F} \rightarrow -j/(200 \cdot 50 \cdot 10^{-6}) = -j100$$

$$0.1 \text{ H} \rightarrow j200 \cdot 0.1 = j20$$

Step 2: Solve using circuit analysis methods

$$50 \parallel -j100 = \frac{(50)(-j100)}{(50 - j100)} = 40 - j20$$

Using voltage divider rule,

$$V_o = \left(\frac{j20}{40 - j20 + 30 + j20} \right) (60 \angle -90^\circ) = 17.14 \angle 0^\circ$$

Step 3: Transform back to time domain


$$V_o = 17.14 \angle 0^\circ, \omega = 200 \frac{\text{rad}}{\text{s}} \rightarrow v_x(t) = 17.14 \cos(200t) \text{ V}$$

2A) Single freq multiple sources example 1

Focus only on STEP 2 (solving by circuit techniques) in this example

Alexander 10.16

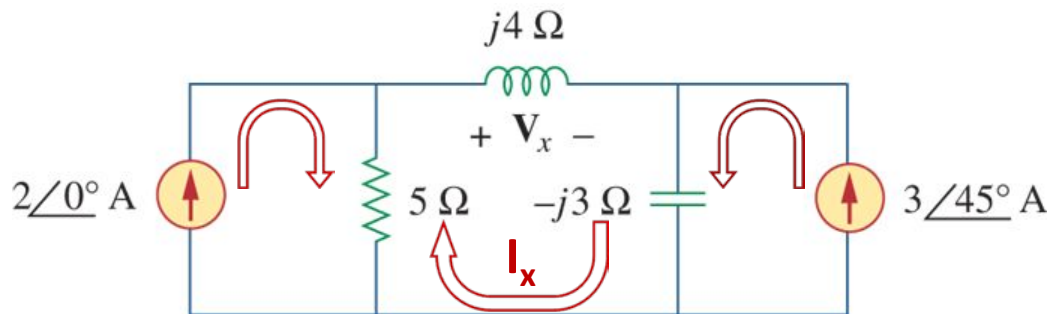Use **MESH CURRENT ANALYSIS** to find V_x



Applying KVL around mesh I_x :

$$I_x(j4 - j3 + 5) - (2\angle 0^\circ)(5) + (3\angle 45^\circ)(-j3) = 0$$


$$\Rightarrow I_x = 1.437\angle 48.94^\circ \text{ A}$$

$$V_x = (1.437\angle 48.94^\circ)(j4) = 5.749\angle 138.94^\circ \text{ V}$$

2B) Single freq multiple sources example 2

Alexander 10.26

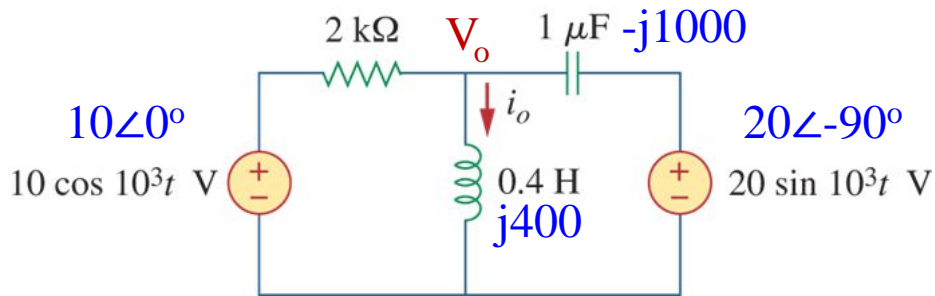Use nodal voltage analysis to find $i_o(t)$



Step 1a: Transform source to phasor

$$10 \cos(10^3 t) \rightarrow 10 \angle 0^\circ, \omega = 10^3 \text{ rad/s}$$

$$20 \sin(10^3 t) \rightarrow 20 \angle -90^\circ, \omega = 10^3 \text{ rad/s}$$

Step 1b: Work out the impedance values

$$1 \mu\text{F} \rightarrow -j/(10^3 * 10^{-6}) = -j1000$$

$$0.4 \text{ H} \rightarrow j10^3 * 0.4 = j400$$

Step 2: Solve using circuit analysis methods

Applying KCL at node V_o :

$$\frac{(10 \angle 0^\circ) - V_o}{2000} + \frac{(20 \angle -90^\circ) - V_o}{-j1000} = \frac{V_o}{j400}$$

$$\Rightarrow V_o = 15.8 \angle 71.57^\circ \text{ V}$$

$$I_o = (15.8 \angle 71.57^\circ) / j400 = 39.5 \angle -18.43^\circ \text{ mA}$$


Step 3: Transform back to time domain

$$I_o = 39.5 \angle -18.43^\circ \text{ mA}, \omega = 10^3 \text{ rad/s} \rightarrow i_o(t) = 39.5 \cos(10^3 t - 18.43^\circ) \text{ mA}$$

3A) Superposition (multiple freq) example 1

Alexander 10.44 (Modified)

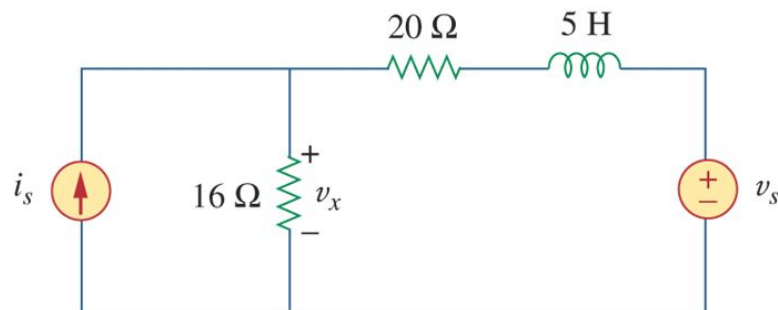Given $v_s(t) = 50\cos(2t)$ and $i_s = 0.9$ A, find $v_x(t)$




Method: Analyze circuit one frequency at a time

In the case, first analyze at DC then at 2 rad/s and then add up the two solutions (**superposition**)

At DC, redraw circuit without $v_s(t)$:

Replace voltage source with short circuit

Replace inductor with short circuit

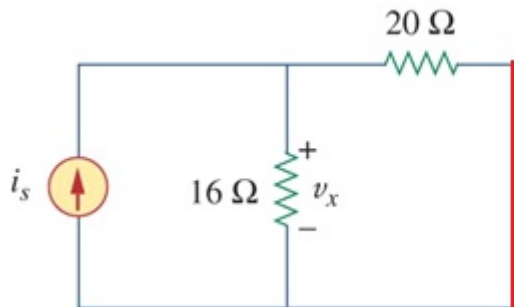


Resistance across current source = $20 \parallel 16 = 80/9\ \Omega$

$V_x = 0.9 * 80/9 = 8\text{ V}$ (**DC**)


3A) Superposition (multiple freq) example 1

Alexander 10.44 (Modified)

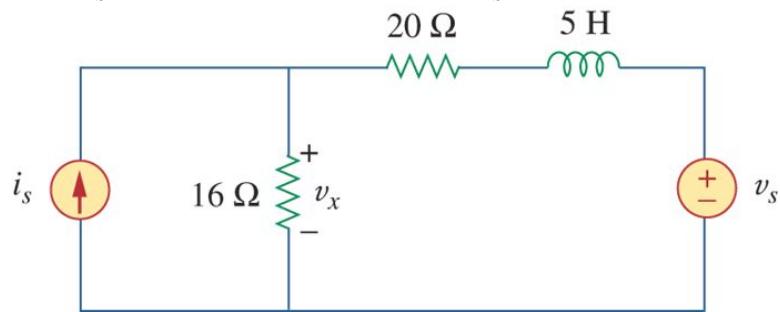Given $v_s(t) = 50\cos(2t)$ and $i_s = 0.9$ A, find $v_x(t)$



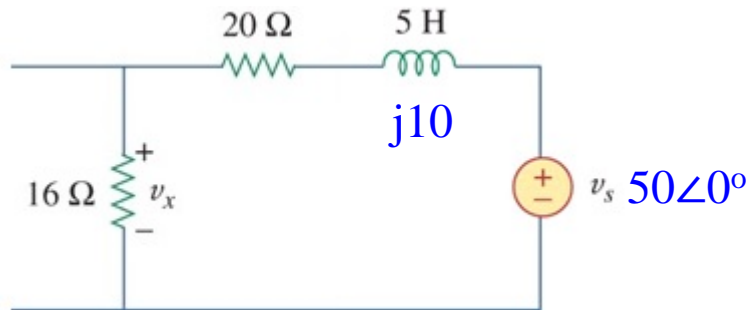At 2 rad/s, redraw circuit without i_s :
Replace current source with open circuit



Final step: Add up both solutions
 $v_x(t) = 21.41\cos(2t - 15.52^\circ) + 8\text{ V}$

Step 1a: Transform source to phasor

$50\cos(2t) \rightarrow 50\angle 0^\circ$, $\omega = 2$ rad/s

Step 1b: Work out the impedance values

$5\text{ H} \rightarrow j2 \cdot 5 = j10$

Step 2: Solve using circuit analysis methods

Using voltage divider rule,

$$\mathbf{V}_x = \left(\frac{16}{16 + 20 + j10} \right) (50\angle 0^\circ) = 21.41\angle -15.52^\circ$$

Step 3: Transform back to time domain

$\mathbf{V}_x = 21.41\angle -15.52^\circ$, $\omega = 2$ rad/s

$\rightarrow v_x(t) = 21.41\cos(2t - 15.52^\circ)\text{ V}$


(NEVER SKIP THIS STEP)

Note that there are 2 terms in the final form (one at DC and another at 2 rad/s)

3B) Superposition (multiple freq) example 2

Alexander 10.45


Find $i(t)$

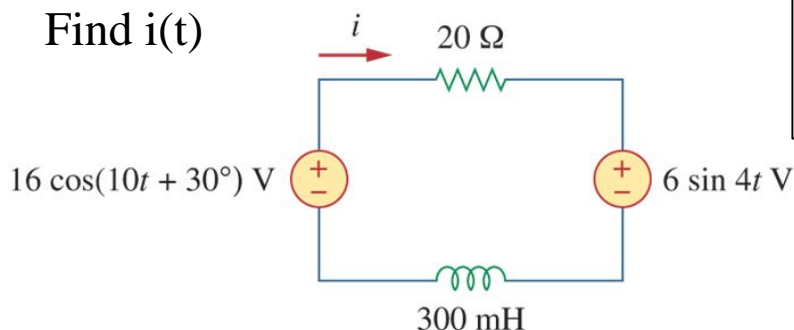

Method: Analyze circuit one frequency at a time
In the case, first analyze at 4 rad/s then 10 rad/s.
Finally, add up the two solutions (**superposition**)

At 4 rad/s, redraw circuit without 10 rad/s source:

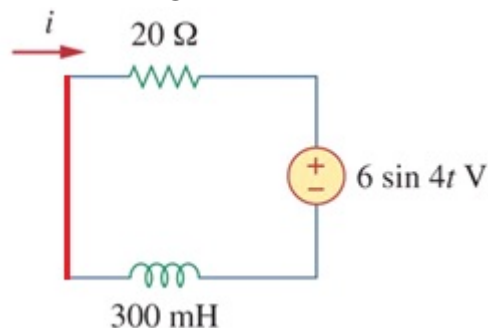Replace 10 rad/s voltage source with short circuit



Step 1a: Transform source to phasor

$$6\sin(4t) \rightarrow 6\angle -90^\circ, \omega = 4 \text{ rad/s}$$

Step 1b: Work out the impedance values

$$300 \text{ mH} \rightarrow j4 \cdot 0.3 = j1.2$$

Step 2: Solve using circuit analysis methods

$$\mathbf{I}^*(20 + j1.2) + 6\angle -90^\circ = 0$$

$$\mathbf{I} = 0.2995\angle 86.57^\circ \text{ A}$$

Step 3: Transform back to time domain

$$\mathbf{I} = 0.2995\angle 86.57^\circ, \omega = 4 \text{ rad/s}$$


$$\rightarrow i(t) = 0.2995 \cos(4t + 86.57^\circ) \text{ A}$$

NEVER SKIP THIS STEP


3B) Superposition (multiple freq) example 2

Alexander 10.45

Find $i(t)$

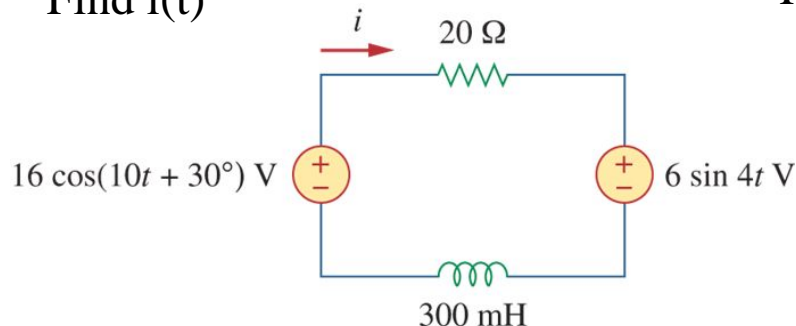

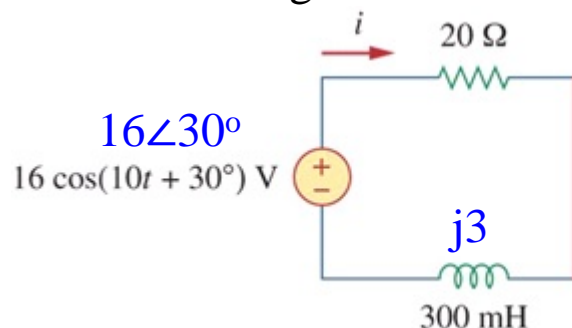At **10** rad/s, redraw circuit without 4 rad/s source:
Replace 4 rad/s voltage source with short circuit



Step 2: Solve using circuit analysis methods

$$\mathbf{I}^*(20 + j3) = 16 \angle 30^\circ$$

$$\mathbf{I} = 0.7911 \angle 21.47^\circ \text{ A}$$

Step 3: Transform back to time domain

$$\mathbf{I} = 0.7911 \angle 21.47^\circ, \omega = 10 \text{ rad/s}$$

$$\rightarrow i(t) = 0.7911 \cos(10t + 21.47^\circ) \text{ A}$$

Step 1a: Transform source to phasor

$$16 \cos(10t + 30^\circ) \rightarrow 16 \angle 30^\circ, \omega = 10 \text{ rad/s}$$

Step 1b: Work out the impedance values

$$300 \text{ mH} \rightarrow j10 * 0.3 = j3$$

NEVER SKIP THIS STEP

Final step: Add up both solutions


$$i(t) = 0.2995 \cos(4t + 86.57^\circ) + 0.7911 \cos(10t + 21.47^\circ) \text{ A}$$

Note that there are 2 terms in the final form
(one at 4 rad/s and another at 10 rad/s)

AC Power: Instantaneous vs. Average

Although the average voltage across a resistor with a sinusoidal AC voltage across it is zero, note that the average power dissipated is not zero. Since $P = V^2/R$, we should consider the square of the voltage.

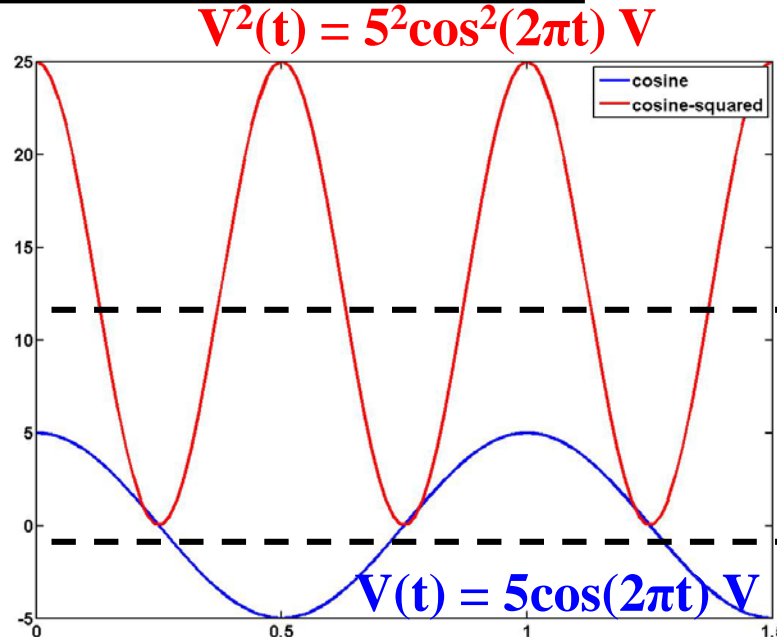The following graph shows the voltage across a 1Ω resistor in blue and the corresponding square of this voltage in red. The red curve therefore shows the **INSTANTANEOUS POWER**.



The instantaneous power is clearly sinusoidal with a DC offset:

$$\begin{aligned} V^2(t) &= 5^2 * 0.5 * (1 + \cos(4\pi t)) \\ &= V_{\text{peak}}^2 * 0.5 * \cos(4\pi t) + \\ &\quad V_{\text{peak}}^2 * 0.5 \\ &= 12.5\cos(4\pi t) + 12.5 \end{aligned}$$

Mean of $V^2 = 12.5$ (DC offset)

Average power of $V^2(t)$ is 12.5 W
Average power of $V^2(t) = 0.5 * V_{\text{peak}}^2$

Mean of $V = 0$