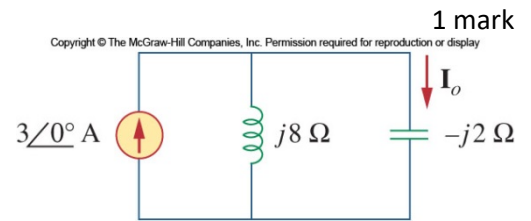



Student ID: _____ Student Name: _____

- 1) Determine the current I_o in the circuit of Fig 1 in phasor form.



1 mark

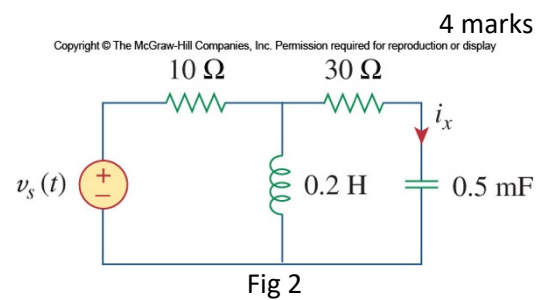- 2) Find $i_x(t)$ in the circuit of Fig 2 in cosine form, given $v_s(t) = 20 \sin(100t - 40^\circ)$ V.



4 marks

- 3) For the circuit in Fig 3 where $i_s = 0.12 \cos(6t + 10^\circ)$ A and $v_s = 9$ V,
- Find v_x at DC;
 - Find $v_x(t)$ at 6 rad/s in cosine form;
 - Hence, find the current through the 16Ω resistor (I_x) at all frequencies;
 - Find the average power consumed by the 16Ω resistor.

5 marks

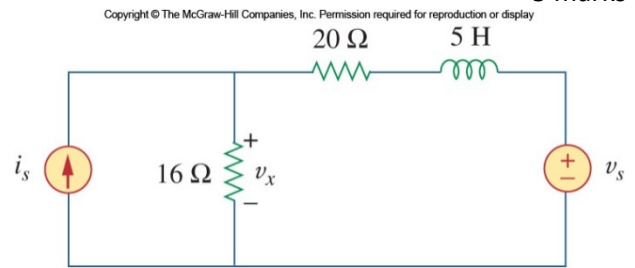


Fig 3