

Q1

$$i_s = 5 \cos(10t + 40^\circ) = 5 \angle 40^\circ$$

$$Z_L = j\omega L = j2 \Omega$$

$$Z_C = \frac{1}{j\omega C} = -j \Omega$$

$$Z_{eq} = \left( \frac{1}{4} + \frac{1}{j2} + \frac{1}{3-j} \right)^{-1}$$

According to ohm's law,  $V = IR = I_s \cdot Z_{eq}$ .

$$V_o = i_s \cdot Z_{eq}$$

$$i_o = \frac{V_o}{3-j} = i_s \cdot \frac{1}{3-j} \cdot \frac{1}{\frac{1}{4} + \frac{1}{j2} + \frac{1}{3-j}} = i_s \cdot \frac{1}{3-j} \cdot \left( \frac{44}{37} + j \frac{32}{37} \right)$$

$$i_o = 2.325 \cos(10t + 94.46^\circ) \quad A$$

Q2.  $V_s(t) = 20 \sin(100t - 40^\circ) = 20 \cos(100t - 130^\circ) = 20 \angle -130^\circ \quad V$

$$Z_L = j\omega L = j20 \Omega$$

$$Z_C = \frac{1}{j\omega C} = -j20 \Omega$$

$$Z_1 = 30 + j20 \Omega$$

$$Z_2 = Z_1 \parallel Z_L = (30 + j20) \parallel j20 = \frac{40}{3} + j20 \Omega$$

Apply voltage divider rule:

$$V_x = \frac{V_s(t) \cdot Z_2}{Z_2 + 10} = 20 \angle -130^\circ \cdot \frac{64}{85} + j \frac{18}{85} = 15.64 \angle -114^\circ V$$

$$i_x = \frac{V_x}{Z_1} = \frac{15.64 \angle -114^\circ}{30 - j20}$$

$$i_x = 0.4338 \cos(100t - 80.6^\circ) \quad A$$


Q3. Apply nodal analysis at node V.

$$\frac{V - (120 \angle -15^\circ)}{40 + j20} + 6 \angle 30^\circ + \frac{V - 0}{-j30} + \frac{V - 0}{50} = 0$$


$$\left( \frac{1}{40 + j20} + \frac{1}{-j30} + \frac{1}{50} \right) V = \frac{120 \angle -15^\circ - 6 \angle 30^\circ}{40 + j20}$$

$$V = \left( \frac{1}{40 + j20} + \frac{1}{-j30} + \frac{1}{50} \right)^{-1} \cdot \left[ \frac{120 \angle -15^\circ}{40 + j20} - 6 \angle 30^\circ \right]$$

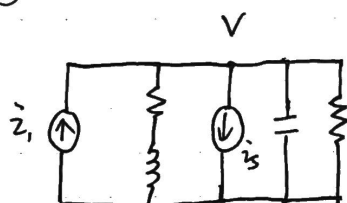Thus, by observation,  $V = (Z_{eq}) \cdot [i_1 - i_s]$



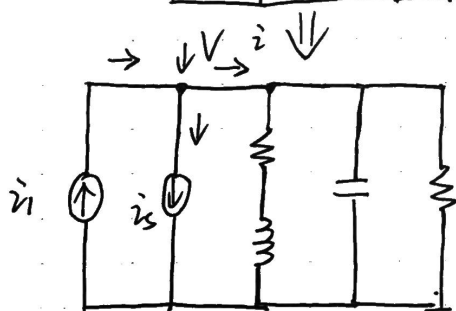
using source transformation.  
Circuit shows the new relationships of two sources.



Focus on the current <sup>flow</sup> of node A, we could find that the current flow to three components is equal to  $i_1 - i_s$ .

$$(i_1 + i_s = i_2)$$

Thus,

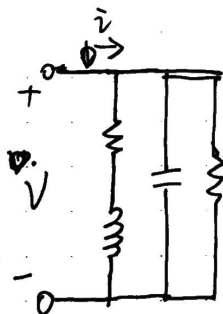

I hope it can help u have more understanding of these kind of question.

Q4  $Z_L = j4 \Omega$   $Z_C = -j2 \Omega$ .

Apply KVL,  $\begin{cases} 10\cos 2t = 4i_1 - j2(i_1 + i_2) & \text{--- ①} \\ 6\sin 2t = j2i_2 - j2(i_1 + i_2) & \text{--- ②} \end{cases}$

①+②, get,

$$10\angle 0^\circ + 6\angle -90^\circ = 4i_1 - j4i_1$$

$$i_1 = \frac{10\angle 0^\circ + 6\angle -90^\circ}{4 - j4} = 2 + j0.5 \text{ A}$$

$$i_2 = -1 + j0.5 \text{ A}$$

$$i = i_1 + i_2 = 1 + j = 1.414 \cos(2t + 45^\circ) \text{ A}$$


For this question, u can also use sources transformation, that trans two voltage sources into two current sources with 3 components (parallel to each other).

Q5. For AC source,

$$V_{s1}(t) = 10\cos 4t \quad V = 10\angle 0^\circ \text{ V}$$


$$Z_L = j4 \quad \frac{2\Omega \parallel Z_L}{Z_{eq}} \cdot \frac{1}{Z_L} = 10\angle 0^\circ \cdot \frac{2 \parallel j4}{2 \parallel j4 + 4} \cdot \frac{1}{j4} = \frac{1}{40} j \frac{3}{40} \text{ A}$$

$$= 0.079 \cos(4t - 71.57^\circ)$$

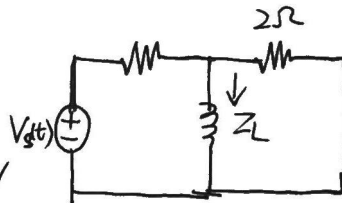


For DC source,
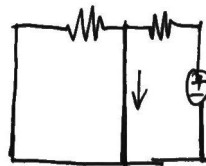
$$i_2 = \frac{V_{oc}}{2\Omega} = \frac{8}{2} = 4 \text{ A}$$



$$i_o = i_2 + i_1 = 4 + 0.079 \cos(4t - 71.57^\circ) \text{ A}$$

Q6 For AC voltage source only.

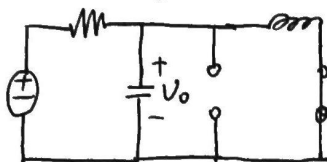


$$V_{ac} = 12 \cos 3t = 12 \angle 0^\circ \text{ V}$$

$$Z_C = \frac{1}{j\omega C} = -j4 \Omega$$

$$Z_L = j\omega L = j6 \Omega$$


$$V_1 = V_{ac} \cdot \frac{Z_C \parallel Z_L}{6 \Omega + Z_C \parallel Z_L} = 12 \angle 0^\circ \cdot \frac{-j12}{6 - j12} = 10.73 \cos(3t - 26.57^\circ) \text{ V}$$

For DC voltage source only.

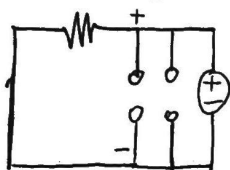

$$V_2 = V_{dc} = 10 \text{ V}$$

For AC current source only.

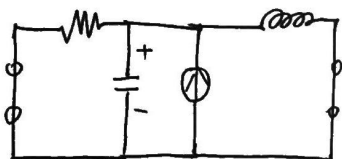

(cosine wave)

$$I_{ac} = 4 \sin 2t = 4 \angle 0^\circ \text{ (This is sine wave)}$$

$$Z_L = j4 \Omega, Z_C = -j6 \Omega$$

$$\rightarrow 4 \cos(2t - 90^\circ) = 4 \angle -90^\circ$$

$$Z_{eq} = \left( \frac{1}{\cancel{6}} + \frac{1}{j4} + \frac{1}{-j6} \right)^{-1} = \cancel{3.6} \text{ } \cancel{j1.2} \text{ } 4.8 + j2.4 \Omega$$

$$V_3 = Z_{eq} \cdot I_{ac} = (4.8 + j2.4) 4 \angle -90^\circ = 21.47 \cos(2t - 63.43^\circ)$$

$$= 21.47 \sin(2t + 26.57^\circ) \text{ V}$$

$$V_0 = V_1 + V_2 + V_3 = 10 + 10.73 \cos(3t - 26.57^\circ) + 21.47 \sin(2t + 26.57^\circ)$$

Q7

For AC voltage source only.



(sin wave).  
 $V_{AC} = 10 \sin(t - 30^\circ) = 10 \angle -30^\circ$   
 $Z_L = j\omega L = j2 \Omega$   
 $Z_C = -j6 \Omega$

$$Z_1 = 4 + Z_L = 4 + j2 \Omega$$


$$Z_2 = 1 + Z_C = 1 - j6 \Omega$$

$$V_1 = V_{AC} \cdot \frac{Z_1 \parallel 2\Omega}{Z_1 \parallel 2\Omega + Z_2} = \frac{1.4 + j0.2}{2.4 - j5.8} = \frac{1.575 + j1.61}{197 - j197} \text{ V}$$

$$i_1 = \frac{V_1}{Z_1} = \frac{1.575 + j1.61}{4 + j2} = 0.5 \sin(t + 49.09^\circ)$$

$$i = \frac{V_1}{Z_1} = \frac{1.575 + j1.61}{4 + j2} = 0.504 \sin(t + 19.1^\circ) \text{ A}$$

For AC current source only.

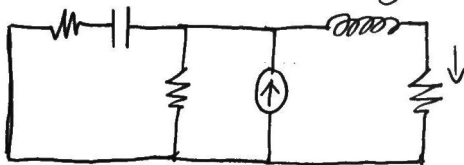

$$I_{AC} = 2 \cos 3t = 2 \angle 0^\circ \text{ A}$$

$$Z_L = j6 \Omega \quad Z_C = -j2 \Omega$$


$$Z_1 = 4 + j6 \Omega$$

$$Z_2 = 1 - j2 \Omega$$

Apply current divider rule:  $i_2 = \frac{\frac{1}{Z_1}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{2}} \cdot I_{AC}$

$$i_2 = \frac{\frac{1}{4 + j6}}{\frac{1}{4 + j6} + \frac{1}{1 - j2} + \frac{1}{2}} \cdot 2 \angle 0^\circ = 0.335 \cos(3t - 76.43^\circ) \text{ A}$$

For DC only.

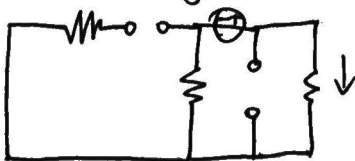

$$i_3 = \frac{V}{R_{eq}} = \frac{24}{2 + 4} = 4 \text{ V}$$

$$i_o = i_3 + i_2 + i_1 = 4 + 0.335 \cos(3t - 76.43^\circ) + 0.504 \sin(t + 19.1^\circ) \text{ A}$$