

**Instructions:** After completing the tutorial assignment, please take a picture of your written solution with your name and student ID at the top of each paper. The CANVAS submission link will be available during the tutorial session only.

1) Find  $i(t)$  in the circuit of Fig 1 for  $t > 0$ .

5 marks

Assume that the switch has been closed for a long time when  $t < 0$ .

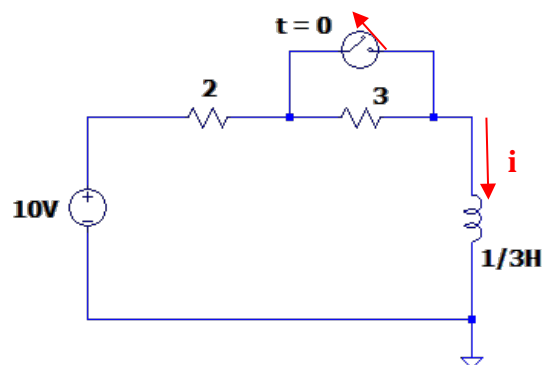


Fig 1

2) The switch in Fig 2 has been in position A for a long time.

5 marks

At  $t = 0$ , the switch moves to B.

i) Determine  $v(t)$  for  $t > 0$ .

ii) Calculate its value at  $t = 1\text{s}$  and  $4\text{s}$ .

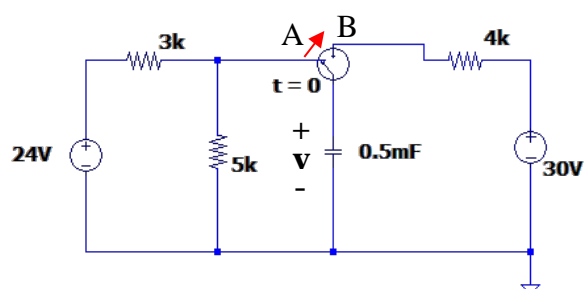


Fig 2

- 3) Find  $v(t)$  for  $t > 0$  in the circuit of Fig 3. Assume the switch has been open for a long time and is closed at  $t=0$ . Calculate  $v(t)$  at  $t = 0.5$ . **5 marks**

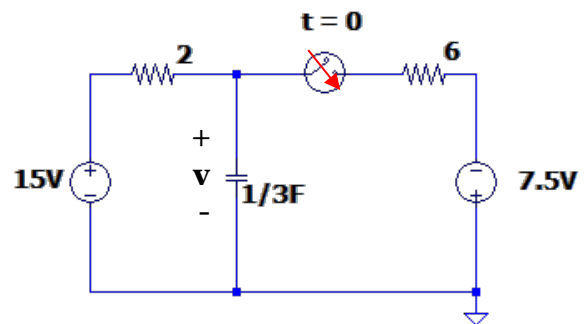


Fig 3